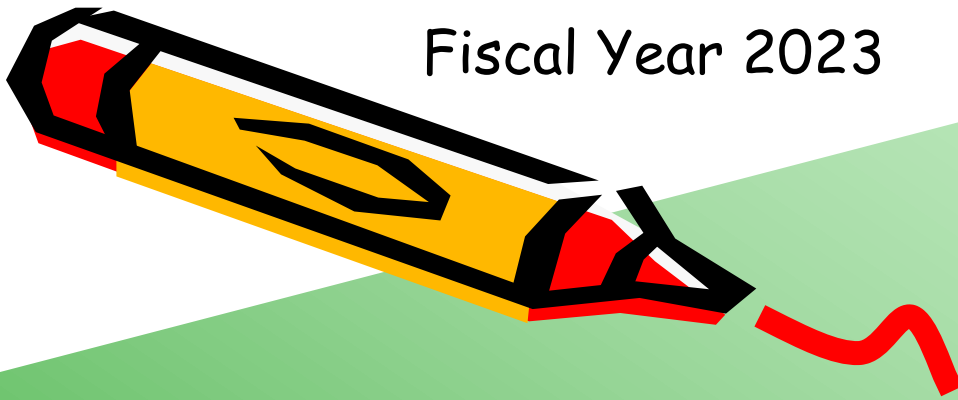


Fiscal Year 2023


Ver. 2023-12-14a



Course number: CSC.T433
School of Computing,
Graduate major in Computer Science

Advanced Computer Architecture

3. HDL, single-cycle processor

 

www.arch.cs.titech.ac.jp/lecture/ACA/
Room No.W834, Lecture (Face-to-face)
Mon 13:30-15:10, Thr 13:30-15:10

Kenji Kise, Department of Computer Science
kise_at_c.titech.ac.jp

(1) Machine Language - **Add** instruction (**add**)

- Instructions are 32 bits long
- Arithmetic Instruction Format (R-type):

add x7, x8, x9



R-type



opcode 7-bits **opcode** that specifies the operation

rs1 5-bits **register** file address of the first **source** operand

rs2 5-bits **register** file address of the second **source** operand

rd 5-bits **register** file address of the result's **destination**

  funct3 and **funct7** 10-bits select the type of operation (**function**)



(2) RISC-V *Add immediate* instruction (*addi*)

- *Small constants* are used often in typical code
- Possible approaches?
 - put “typical constants” in memory and load them
 - create hard-wired registers (like x0) for constants like 1
 - *have special instructions that contain constants !*

`addi x7, x8, -2` # x7 = x8 + (-2)

- Machine format (I format):




- The constant is kept inside the instruction itself
 - Immediate format limits values to the range $+2^{11}-1$ to -2^{11}

(3) Machine Language - Load word instruction (lw)

- Load Instruction Format (I-type):

lw x5, 8(x7)

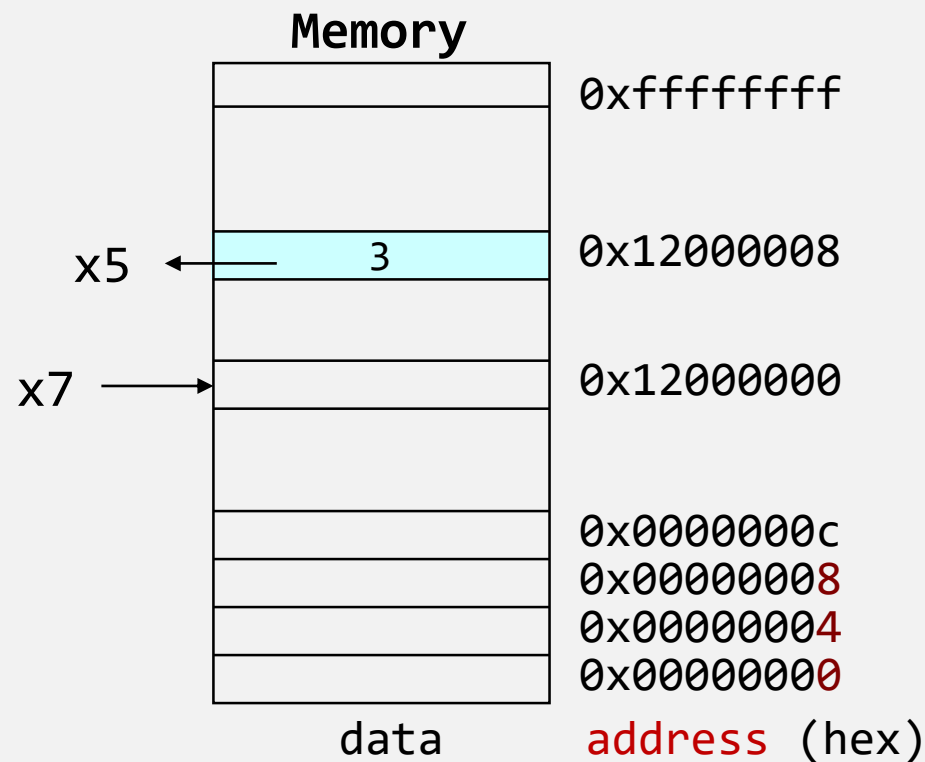



(4) Machine Language - Store word instruction (sw)

- Load Instruction Format (S-type):

sw x5, 8(x7)



S-type

  

(5) RISC-V branch if not equal instructions (bne)

- RISC-V conditional branch instructions (bne, branch if not equal):


```
bne x4, x5, Lb1 # go to Lb1 if x4!=x5
```

Ex: `if (i==j) h = i + j;`


```
bne x4, x5, Lb11 # if (i!=j) goto Lb11
add x6, x4, x5   # h = i + j;
```

`Lb11: ...`

- Instruction Format (B-type):

 

 - How is the branch destination address specified?



Sample assembly code in RISC-V

- sample assembly code in RISC-V with `add`, `addi`, `lw`, `sw`, `bne` instructions
- the leftmost number is the instruction memory address where the instruction is stored
- the first register `x0` is zero register with hardwiring 0


```
0x00  L1: addi x5, x0, 2      # x5 = 2
0x04      addi x6, x0, 3      # x6 = 3
0x08      add  x7, x5, x6      # x7 = x5 + x6 = 5
0x0c      sw   x7, 32(x0)     # mem[0 + 32] = x7 = 5
0x10      lw   x8, 32(x0)     # x8 = mem[0 + 32]
0x14      add  x9, x8, x5      # x9 = x8 + x5 = 7
0x18      bne  x5, x6, L1     # go to L1 if x5!=x6
```

```
0x00200293
0x00300313
0x006283B3
0x02702023
0x02002403
0x005404B3
0xFE6294E3
```




Sample circuit 3

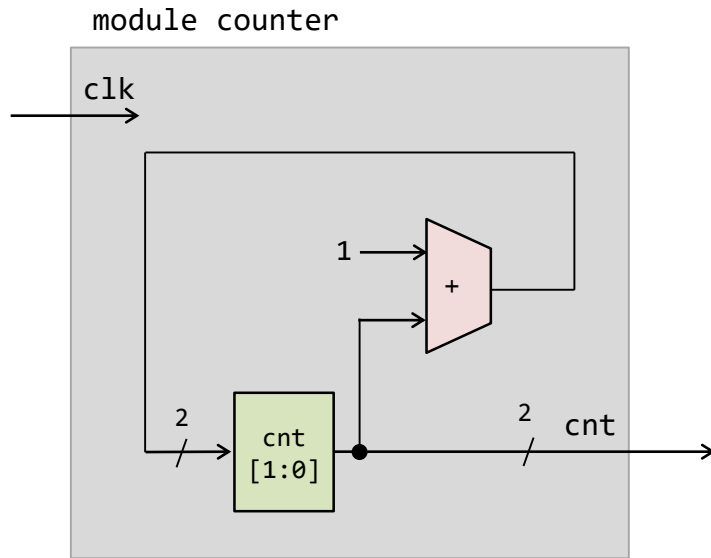- 2-bit counter as a simple *sequential circuit*




```
module top();  
  reg r_clk=0;  
  initial #150 forever #50 r_clk = ~r_clk;  
  initial #810 $finish;  
  wire [1:0] w_cnt;  
  counter m1 (r_clk, w_cnt);  
  initial $dumpvars(0, m1);  
endmodule
```
 
```
module counter(clk, cnt);  
  input wire clk;  
  output reg [1:0] cnt;  
  initial cnt = 0;  
  always@(posedge clk) cnt <= cnt + 1;  
endmodule
```



Single-cycle implementation of processors

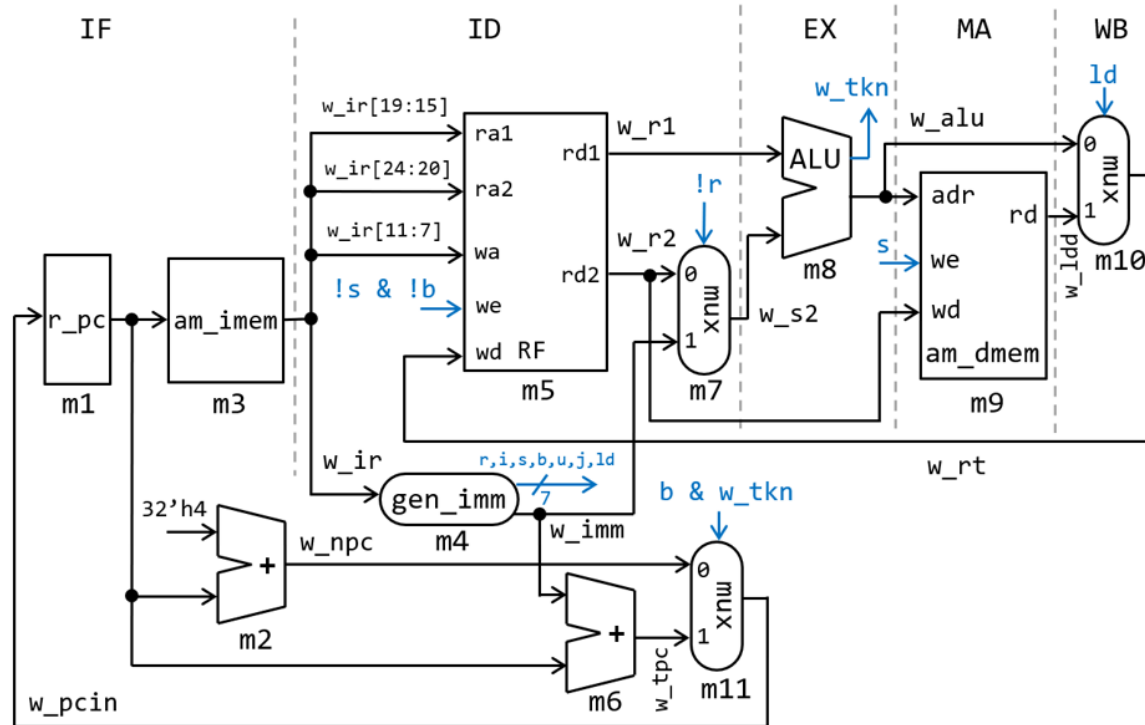- Single-cycle implementation also called **single clock cycle implementation** is the implementation in which an instruction is executed in one clock cycle. While easy to understand, it is too slow to be practical.




Steps in processing an instruction

- **IF: Instruction Fetch**
fetch an instruction from **instruction memory** or instruction cache
- **ID: Instruction Decode**
decode an instruction and read input operands from **register file**
- **EX: Execution**
perform operation, calculate an address of lw/sw
- **MEM: Memory Access**
access **data memory** or data cache for lw/sw
- **WB: Write Back**
write operation result and loaded data to register file




Multiplexer (MUX)

 - The multiplexer, shortened to MUX, is a combinational logic circuit designed to switch one of several input lines through to a single common output line by a control signal.




c	a	b	d
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 
```
1 module m_mux(a, b, c, d);  
2   input wire a, b, c;  
3   output wire d;  
4   assign d = (c) ? b : a; # ternary operator  
5 endmodule
```



 Instruction and data memory in Verilog HDL



 
```
1 module m_am_imem(w_pc, w_insn);
2   input  wire [31:0] w_pc;
3   output wire [31:0] w_insn;
4   reg [31:0] mem [0:63];
5   assign w_insn = mem[w_pc[7:2]];
6   integer i; initial for (i=0; i<64; i=i+1) mem[i] = 0;
7 endmodule
```




```
1 module m_am_dmem(w_clk, w_adr, w_we, w_wd, w_rd);
2   input  wire w_clk, w_we;
3   input  wire [31:0] w_adr, w_wd;
4   output wire [31:0] w_rd;
5   reg [31:0] mem [0:63];
6   assign w_rd = mem[w_adr[7:2]];
7   always @(posedge w_clk) if (w_we) mem[w_adr[7:2]] <= w_wd;
8   integer i; initial for (i=0; i<64; i=i+1) mem[i] = 0;
9 endmodule
```



Register file (RF) in Verilog HDL (1)

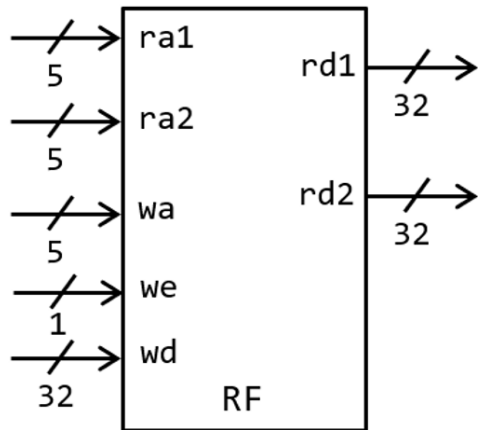

```
1 module m_RF(w_clk, w_ra1, w_ra2, w_rd1, w_rd2, w_wa, w_we, w_wd);
2   input wire w_clk, w_we;
3   input wire [4:0] w_ra1, w_ra2, w_wa;
4   output wire [31:0] w_rd1, w_rd2;
5   input wire [31:0] w_wd;
6   reg [31:0] mem [0:31];
7   assign w_rd1 = (w_ra1==0) ? 0 : mem[w_ra1];
8   assign w_rd2 = (w_ra2==0) ? 0 : mem[w_ra2];
9   always @(posedge w_clk) if (w_we) mem[w_wa] <= w_wd;
10  integer i; initial for (i=0; i<32; i=i+1) mem[i] = 0;
11 endmodule
```

 


```
1 module m_RF(w_clk, w_ra1, w_ra2, w_rd1, w_rd2, w_wa, w_we, w_wd);
2   input wire w_clk, w_we;
3   input wire [4:0] w_ra1, w_ra2, w_wa;
4   output wire [31:0] w_rd1, w_rd2;
5   input wire [31:0] w_wd;
6   reg [31:0] mem [0:31];
7   assign w_rd1 = (w_ra1==0) ? 0 : mem[w_ra1];
8   assign w_rd2 = (w_ra2==0) ? 0 : mem[w_ra2];
9   always @(posedge w_clk) if (w_we) mem[w_wa] <= w_wd;
10  integer i; initial for (i=0; i<32; i=i+1) mem[i] = 0;
11 endmodule
```

first read port




Register file (RF) in Verilog HDL (2)

 


```
1 module m_RF(w_clk, w_ra1, w_ra2, w_rd1, w_rd2, w_wa, w_we, w_wd);
2   input wire w_clk, w_we;
3   input wire [4:0] w_ra1, w_ra2, w_wa;
4   output wire [31:0] w_rd1, w_rd2;
5   input wire [31:0] w_wd;
6   reg [31:0] mem [0:31];
7   assign w_rd1 = (w_ra1==0) ? 0 : mem[w_ra1];
8   assign w_rd2 = (w_ra2==0) ? 0 : mem[w_ra2];
9   always @(posedge w_clk) if (w_we) mem[w_wa] <= w_wd;
10  integer i; initial for (i=0; i<32; i=i+1) mem[i] = 0;
11 endmodule
```

second read port

 

```
1 module m_RF(w_clk, w_ra1, w_ra2, w_rd1, w_rd2, w_wa, w_we, w_wd);
2   input wire w_clk, w_we;
3   input wire [4:0] w_ra1, w_ra2, w_wa;
4   output wire [31:0] w_rd1, w_rd2;
5   input wire [31:0] w_wd;
6   reg [31:0] mem [0:31];
7   assign w_rd1 = (w_ra1==0) ? 0 : mem[w_ra1];
8   assign w_rd2 = (w_ra2==0) ? 0 : mem[w_ra2];
9   always @(posedge w_clk) if (w_we) mem[w_wa] <= w_wd;
10  integer i; initial for (i=0; i<32; i=i+1) mem[i] = 0;
11 endmodule
```

write port

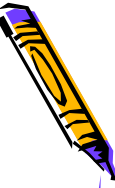


proc02: single cycle proc. supporting add

```

1 module m_proc2(w_clk);
2   input wire w_clk;
3   wire [31:0] w_npc, w_ir, w_r1, w_r2, w_rt;
4   reg [31:0] r_pc = 0; // m1
5   assign w_npc = r_pc + 4; // m2
6   m_am_imem m3 (r_pc, w_ir);
7   m_RF m4 (w_clk, w_ir[19:15], w_ir[24:20], w_r1, w_r2, w_ir[11:7], 1, w_rt);
8   assign w_rt = w_r1 + w_r2; // m5
9   always @(posedge w_clk) r_pc <= w_npc; // m1
11 endmodule

```

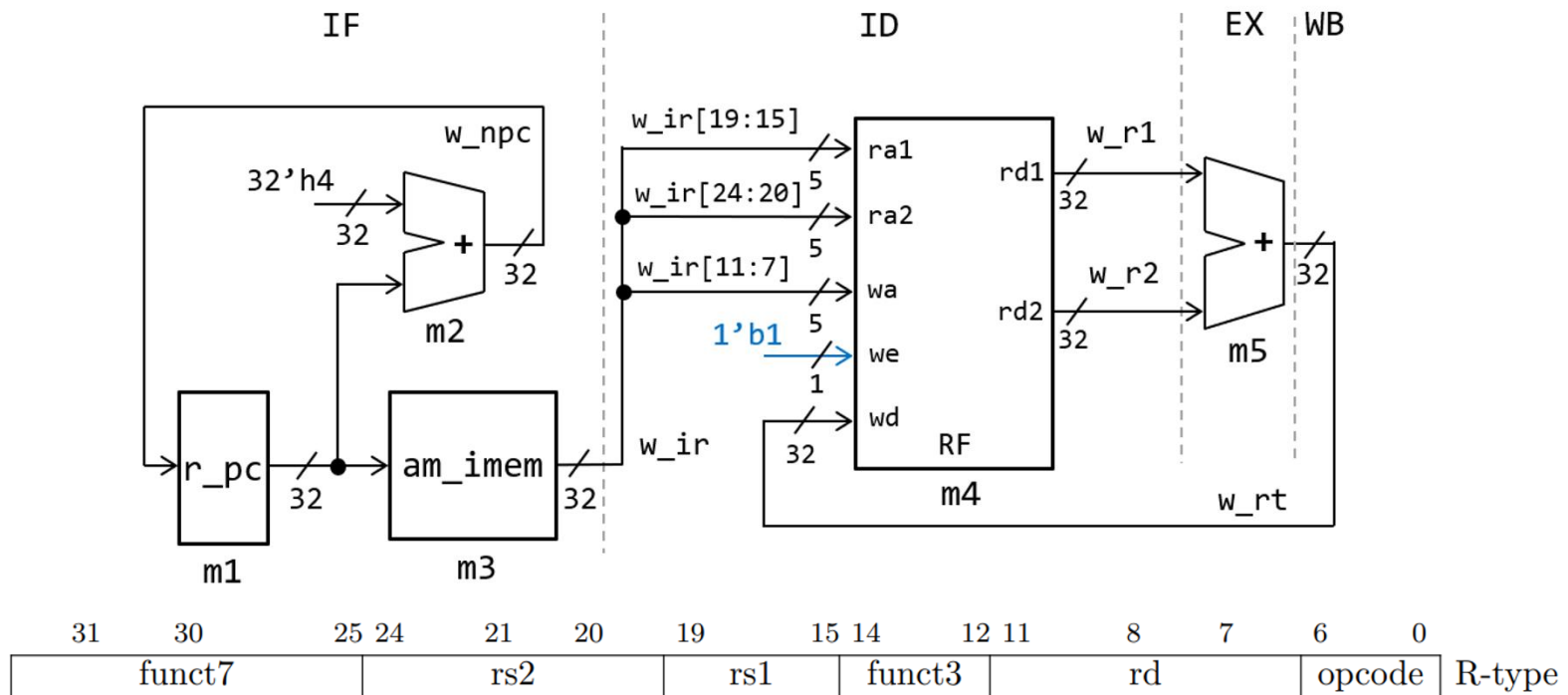

immediate generation module (**gen_imm**)

 
 


Figure 2.3: RISC-V base instruction formats showing immediate variants.

```

1 module m_get_type(opcode5, r, i, s, b, u, j);
2   input wire [4:0] opcode5;
3   output wire r, i, s, b, u, j;
4   assign j = (opcode5==5'b11011);
5   assign b = (opcode5==5'b11000);
6   assign s = (opcode5==5'b01000);
7   assign r = (opcode5==5'b01100);
8   assign u = (opcode5==5'b01101 || opcode5==5'b00101);
9   assign i = ~(j | b | s | r | u);
10  endmodule

1 module m_get_imm(ir, i, s, b, u, j, imm);
2   input wire [31:0] ir;
3   input wire i, s, b, u, j;
4   output wire [31:0] imm;
5   assign imm= (i) ? {{20{ir[31]}},ir[31:20]} :
6               (s) ? {{20{ir[31]}},ir[31:25],ir[11:7]} :
7               (b) ? {{20{ir[31]}},ir[7],ir[30:25],ir[11:8],1'b0} :
8               (u) ? {ir[31:12],12'b0} :
9               (j) ? {{12{ir[31]}},ir[19:12],ir[20],ir[30:21],1'b0} : 0;
10  endmodule


1 module m_gen_imm(w_ir, w_imm, w_r, w_i, w_s, w_b, w_u, w_j, w_ld);
2   input wire [31:0] w_ir;
3   output wire [31:0] w_imm;
4   output wire w_r, w_i, w_s, w_b, w_u, w_j, w_ld;
5   m_get_type m1 (w_ir[6:2], w_r, w_i, w_s, w_b, w_u, w_j);
6   m_get_imm m2 (w_ir, w_i, w_s, w_b, w_u, w_j, w_imm);
7   assign w_ld = (w_ir[6:2]==0);
8   endmodule

```



proc03: single cycle proc. supporting add, addi

```
1 module m_proc3(w_clk);
2   input wire w_clk;
3   wire [31:0] w_npc, w_ir, w_imm, w_r1, w_r2, w_s2, w_rt;
4   wire w_r, w_i, w_s, w_b, w_u, w_j, w_ld;
5   reg [31:0] r_pc = 0; // m1
6   assign w_npc = r_pc + 4; // m2
7   m_am_imem m3 (r_pc, w_ir);
8   m_gen_imm m4 (w_ir, w_imm, w_r, w_i, w_s, w_b, w_u, w_j, w_ld);
9   m_RF m5 (w_clk, w_ir[19:15], w_ir[24:20], w_r1, w_r2, w_ir[11:7], 1, w_rt);
10  assign w_s2 = (w_i) ? w_imm : w_r2; // m6
11  assign w_rt = w_r1 + w_s2; // m7
12  always @(posedge w_clk) r_pc <= w_npc; // m1
13 endmodule
```

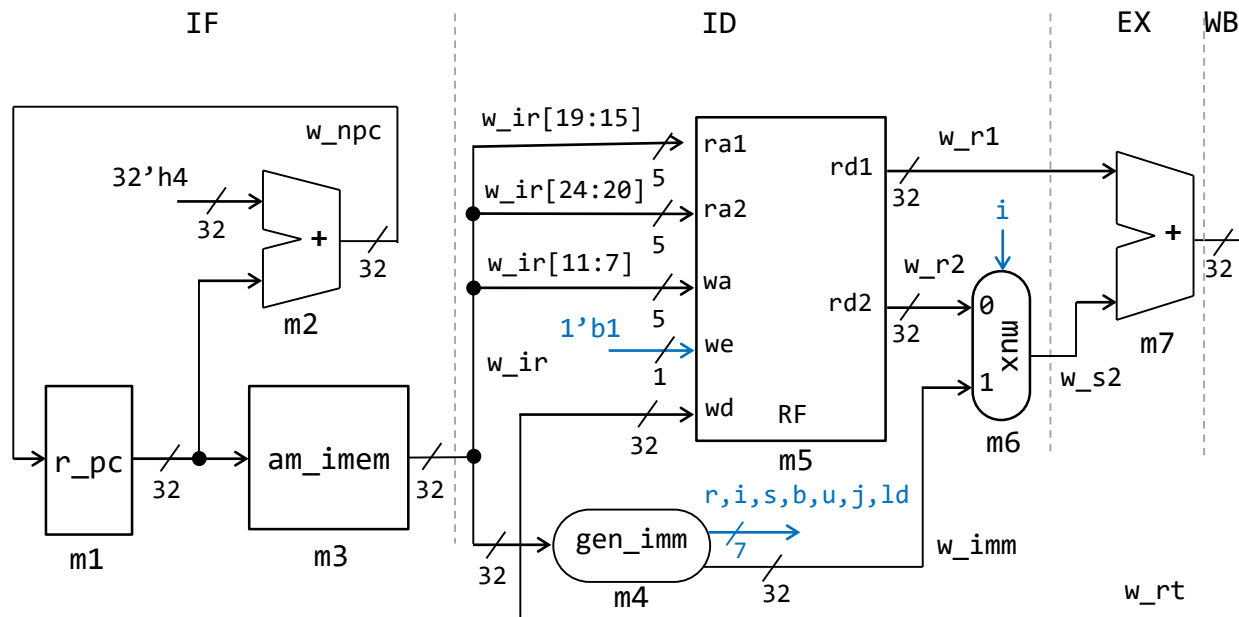


proc04: single cycle proc. supporting add, addi, lw, sw

```

1 module m_proc4(w_clk);
2   input wire w_clk;
3   wire [31:0] w_npc, w_ir, w_imm, w_r1, w_r2, w_s2, w_rt;
4   wire [31:0] w_alu, w_ldd;
5   reg [31:0] r_pc = 0;
6   wire w_r, w_i, w_s, w_b, w_u, w_j, w_ld;
7   assign w_npc = r_pc + 4;
8   m_am_imem m3 (r_pc, w_ir);
9   m_gen_imm m4 (w_ir, w_imm, w_r, w_i, w_s, w_b, w_u, w_j, w_ld);
10  m_RF m5 (w_clk, w_ir[19:15], w_ir[24:20], w_r1, w_r2, w_ir[11:7], !w_s, w_rt);
11  assign w_s2 = (!w_r) ? w_imm : w_r2;
12  assign w_alu = w_r1 + w_s2;
13  m_am_dmem m8 (w_clk, w_alu, w_s, w_r2, w_ldd);
14  assign w_rt = (w_ld) ? w_ldd : w_alu;
15  always @(posedge w_clk) r_pc <= w_npc;
16 endmodule

```

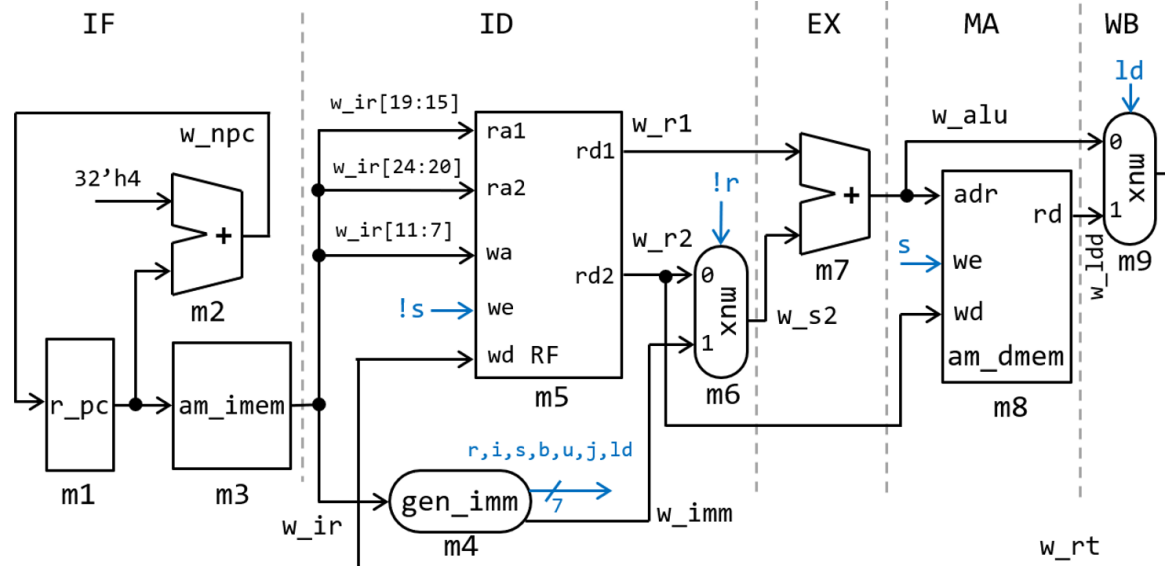


proc05: single cycle proc. supporting add, addi, lw, sw, bne



```

1 module m_proc5(w_clk);
2   input wire w_clk;
3   wire [31:0] w_npc, w_ir, w_imm, w_r1, w_r2, w_s2, w_rt;
4   wire [31:0] w_alu, w_ldd, w_tpc, w_pcin;
5   wire w_tkn;
6   reg [31:0] r_pc=0;
7   assign w_pcin = (w_b & w_tkn) ? w_tpc : w_npc;    # m11
8   assign w_npc = r_pc + 4;
9   m_am_imem m3 (r_pc, w_ir);
10  wire w_r, w_i, w_s, w_b, w_u, w_j, w_ld;
11  m_gen_imm m4 (w_ir, w_imm, w_r, w_i, w_s, w_b, w_u, w_j, w_ld);
12  m_RF m5 (w_clk, w_ir[19:15], w_ir[24:20], w_r1, w_r2, w_ir[11:7], !w_s & !w_b, w_rt);
13  assign w_tpc = r_pc + w_imm;    # m6
14  assign w_s2 = (!w_r & !w_b) ? w_imm : w_r2;
15  assign w_alu = w_r1 + w_s2;    # m8
16  assign w_tkn = w_r1 != w_s2;    # m8
17  m_am_dmem m9 (w_clk, w_alu, w_s, w_r2, w_ldd);
18  assign w_rt = (w_ld) ? w_ldd : w_alu;
19  always @(posedge w_clk) r_pc <= w_pcin;
20 endmodule

```

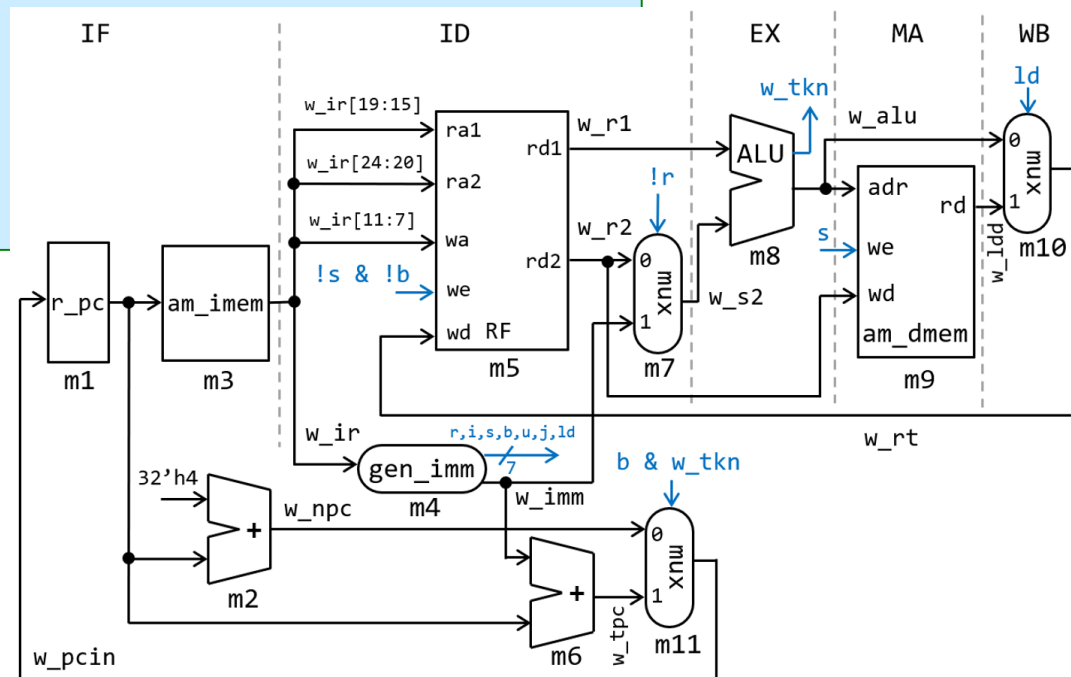


proc05: single cycle proc. supporting add, addi, lw, sw, bne




```

 0x00 L1: addi x5, x0, 2    # x5 = 2
0x04  addi x6, x0, 3    # x6 = 3
0x08  add  x7, x5, x6    # x7 = x5 + x6 = 5
0x0c  sw   x7, 32(x0)    # mem[0 + 32] = x7 = 5
0x10  lw   x8, 32(x0)    # x8 = mem[0 + 32]
0x14  add  x9, x8, x5    # x9 = x8 + x5 = 7
0x18  bne  x5, x6, L1    # go to L1 if x5!=x6
    
```




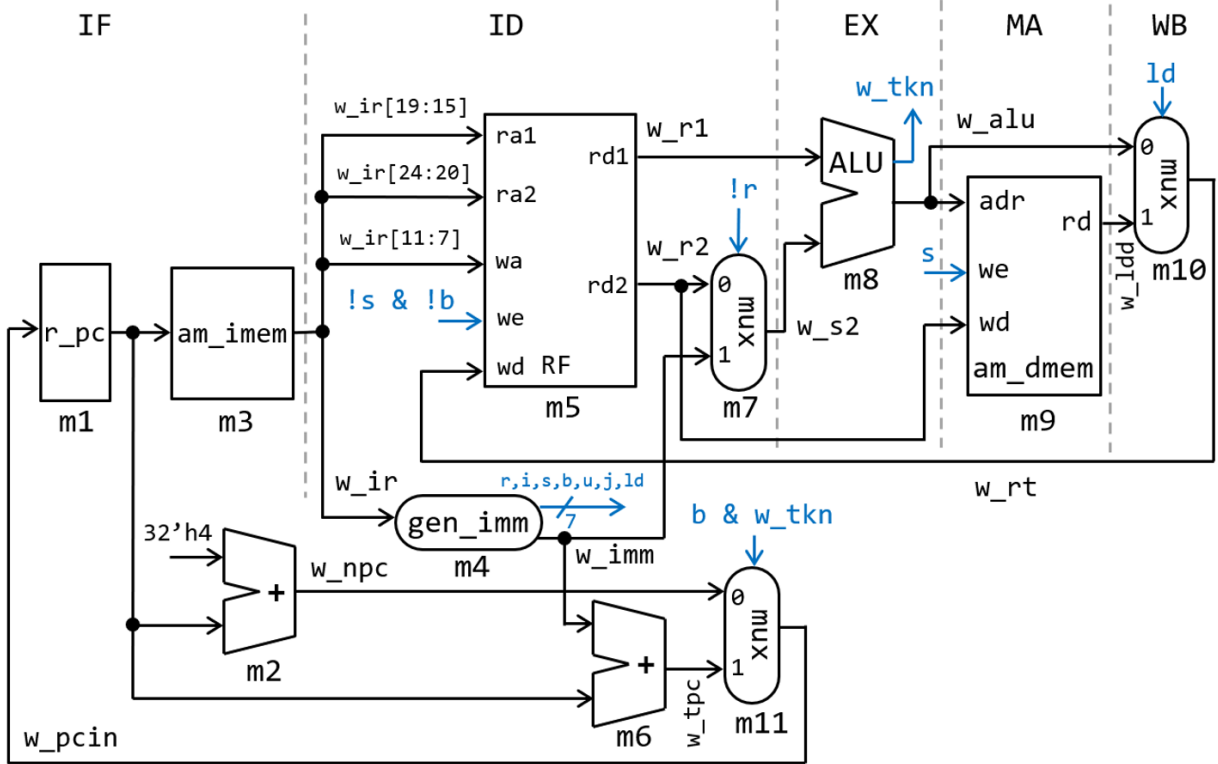R-type for *add*, I-type for *addi* and *lw*, S-type for *sw*, and B-type for *bne*



Processing behavior of proc4


- executing `addi x1, x0, 7` of address `0x00`

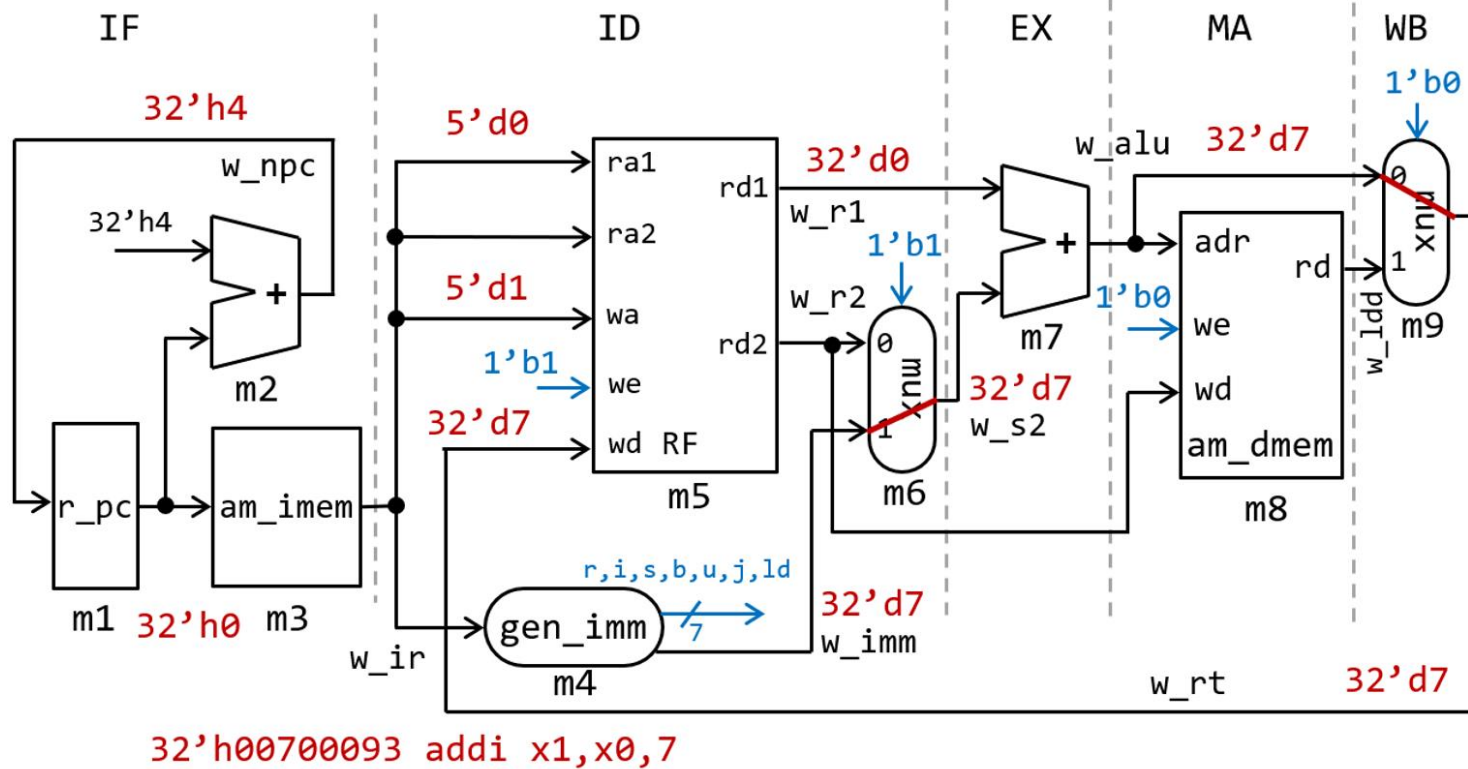

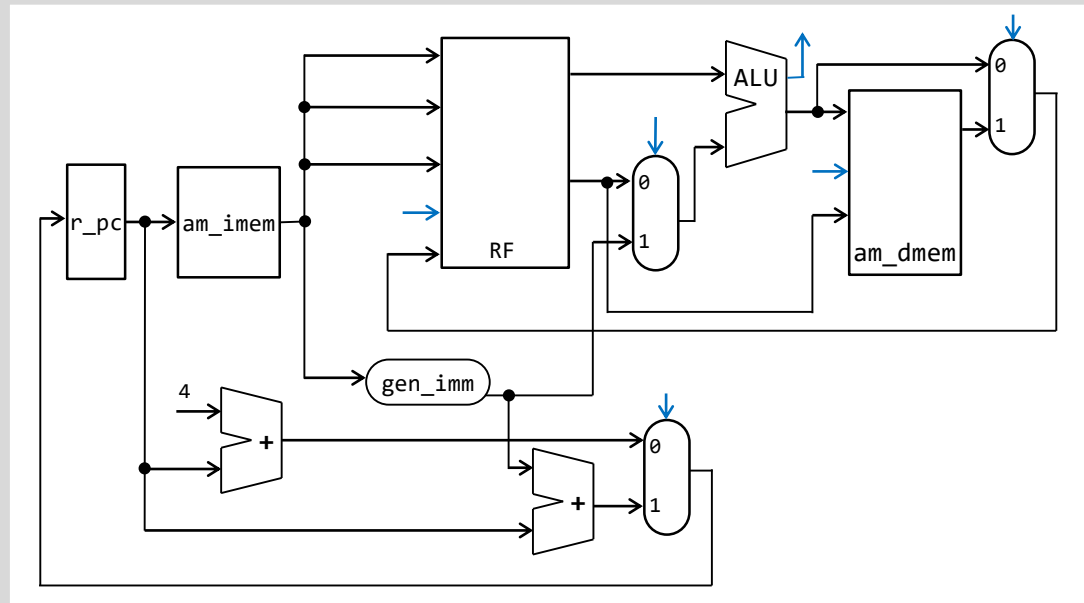Exercise 1



- Draw a block diagram of the processor **proc05** and write the valid values on wires when the processor is executing the **lw** instruction

```
0x00 L1: addi x5, x0, 2      # x5 = 2
0x04      addi x6, x0, 3      # x6 = 3
0x08      add  x7, x5, x6      # x7 = x5 + x6 = 5
0x0c      sw   x7, 32(x0)      # mem[0 + 32] = x7 = 5
0x10      lw   x8, 32(x0)      # x8 = mem[0 + 32]
0x14      add  x9, x8, x5      # x9 = x8 + x5 = 7
0x18      bne  x5, x6, L1      # go to L1 if x5!=x6
```



Critical path of proc5

- It is too slow to be practical.

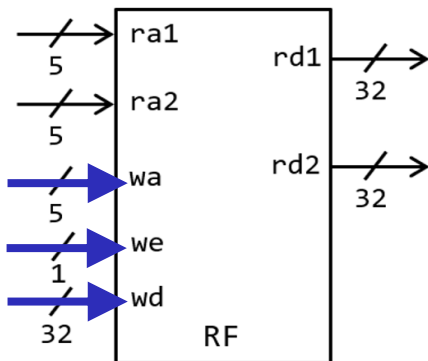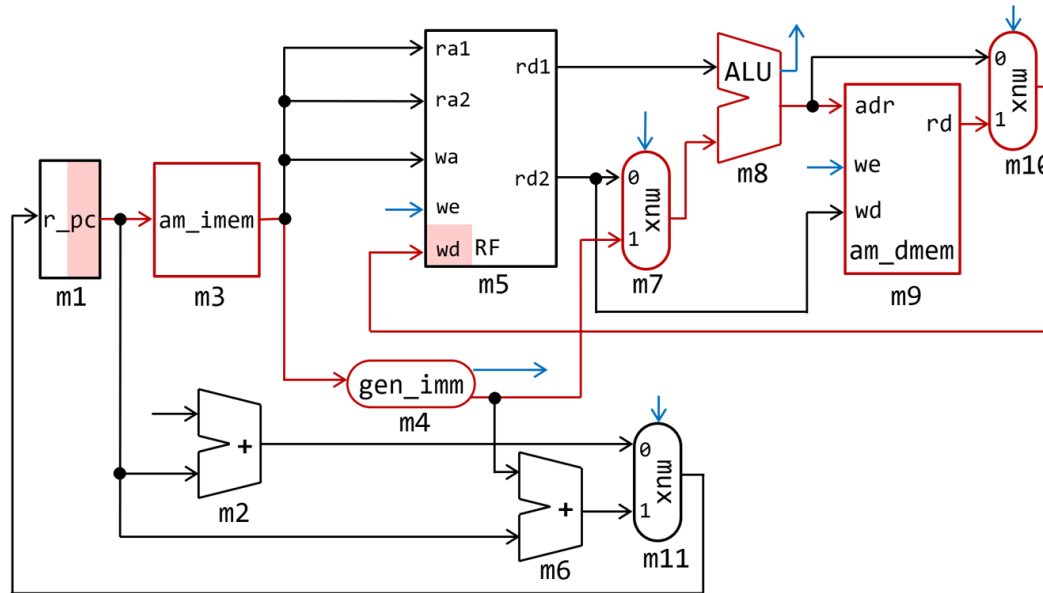

write port

```

1 module m_RF(w_clk, w_ra1, w_ra2, w_rd1, w_rd2, w_wa, w_we, w_wd);
2   input wire w_clk, w_we;
3   input wire [4:0] w_ra1, w_ra2, w_wa;
4   output wire [31:0] w_rd1, w_rd2;
5   input wire [31:0] w_wd;
6   reg [31:0] mem [0:31];
7   assign w_rd1 = (w_ra1==0) ? 0 : mem[w_ra1];
8   assign w_rd2 = (w_ra2==0) ? 0 : mem[w_ra2];
9   always @(posedge w_clk) if (w_we) mem[w_wa] <= w_wd;
10  integer i; initial for (i=0; i<32; i=i+1) mem[i] = 0;
11 endmodule

```



Clock rate is mainly determined by

- **Switching speed of gates (transistors)**
- **The number of levels of gates**
 - The maximum number of gates cascaded in series in any combinational logics.
 - In this example, the number of levels of gates is 3.
- **Wiring delay and fanout**

