

Department of Computer Science
Course number: CSC.T341



コンピュータ論理設計 Computer Logic Design

5. VLSIとリコンフィギャラブルシステム VLSI and Reconfigurable Systems

吉瀬 謙二 情報工学系


Kenji Kise, Department of Computer Science

kise_at_c.titech.ac.jp www.arch.cs.titech.ac.jp/lecture/CLD/

講義: 月曜日 10:45-12:25, 木曜日 10:45-12:25

コンピュータ論理設計の特徴

 
- 講義2単位, 演習1単位.
- **1人1台のFPGA (Field-Programmable Gate Array) ボードを用いた演習.**
- 4人程度を1グループとした共同作業と問題解決.
- 教科書で説明されるプロセッサのRISC-V版をハードウェア記述言語Verilog HDLで記述し, FPGAボードに実装する.
- グループとしてプロセッサの高速化に取り組み, コンテスト形式で成果を競う.
- 3Q開講のコンピュータアーキテクチャ(CSC.T363)のための準備.



```
module main (clk, led);
  input wire clk;
  output wire led;

  reg [26:0] cnt=0;
  always @(posedge clk) cnt <= cnt + 1;

  assign led = cnt[26];
endmodule
```

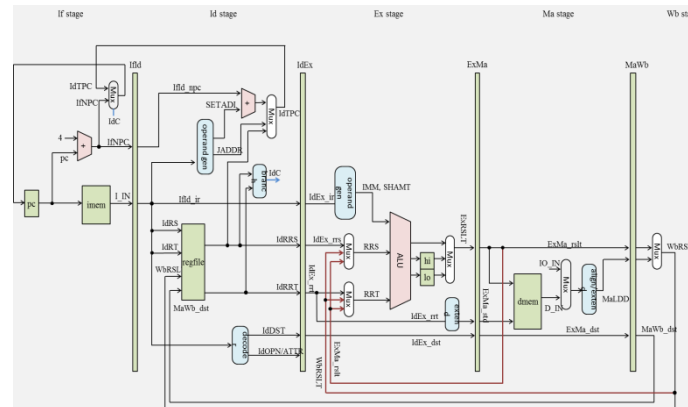


ASIC (Application Specific Integrated Circuit)

- ASIC (特定用途向け集積回路)
 - マイクロプロセッサとしてのASIC
 - FPGAとしてのASIC
- **FPGAとしてのASIC**に実現されるマイクロプロセッサは？




Intel Skylake microprocessor August 2015

 

Xilinx Artix-7 FPGA on Arty A7-35T

Reconfigurable Systems

 - 再構成可能(リコンフィギュラブル)システム
 - 問題の解法アルゴリズムをハードウェア化してユーザが書き換え可能なデバイス上で直接実行することにより, 高い性能と柔軟性を実現するシステム
 - 書き換え可能なデバイスを活用するコンピューティングシステムをアダプティブコンピューティングと呼ぶ.
- FPGA (Field Programmable Gate Array)
 - AMD (Xilinx)
 - Intel (Altera)
 - Lattice
 - NanoBridge






This circuit can change the role of AND or OR gate by the value stored in s .
Is this reconfigurable? No!




制御信号cによってANDゲートあるいはORゲートとなる回路

   - ANDゲートとORゲートを切り替えることで性能が向上する例を考える.
- レジスタの値で出力を選択する回路
- この例は、再構成可能システムではない！







ルックアップテーブル (Lookup Table, LUT)

 - a, b を入力として, c を出力とする LUT
- 値を保持するレジスタ(黄色)の値を選択する回路



2入力のLUTの構成

    


入力		出力
a	b	c
0	0	r1
0	1	r2
1	0	r3
1	1	r4



ルックアップテーブル (Lookup Table, LUT)

 
- レジスタの値を上から 0, 1, 1, 1 に設定すると、このLUTはORゲートと同じ動作をする。



2入力のLUT


a	b	c
0	0	0
0	1	1
1	0	1
1	1	1

真理値表

 

左の構成のLUTと等価な回路

 
- レジスタの値を上から 0, 0, 0, 1 に設定すると、このLUTはANDゲートと同じ動作をする。



2入力のLUT

a	b	c
0	0	0
0	1	0
1	0	0
1	1	1


真理値表

 

左の構成のLUTと等価な回路

ルックアップテーブル (Lookup Table, LUT)

- Reconfigurable Logic

 


This circuit can change the role of AND or OR gate by the value stored in s .

Is this reconfigurable?


No!

3-input LUT structure

 


ルックアップテーブル (Lookup Table, LUT)

 - Reconfigurable Logic
 - 3-input LUT has 8 configuration registers
 - 6-input LUT for Artix-7 FPGA




Truth table

a	b	cin	s
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

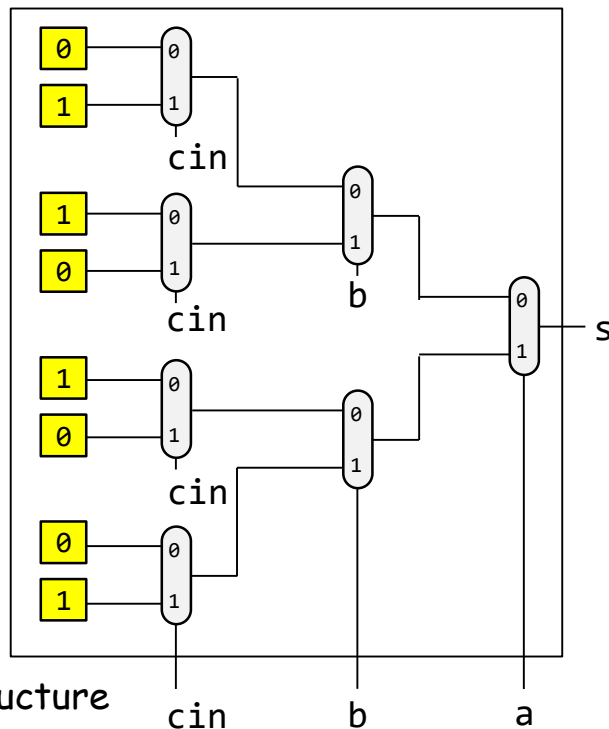

3-input LUT structure

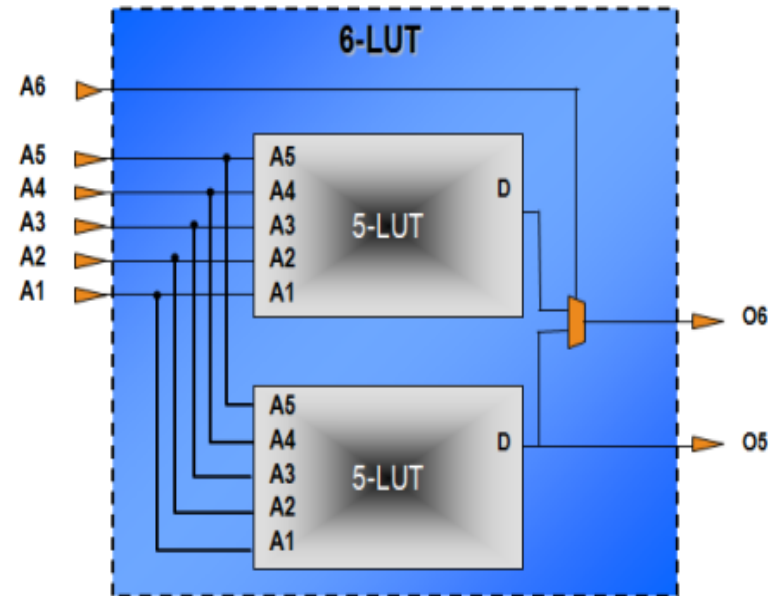


6-input LUT for Artix-7 FPGA




FPGA (Field Programmable Gate Array)

 - Artix-7 FPGA (xc7a35tcsg324-1L)
- Vivado, **open implemented design**, and select **Layout Menu**, then **I/O planning**
 - $16 \times 16 = 324$ pins, max user pins of 250



FPGA chip photo


 


main11.xdcの最初の2行

```
set_property -dict { PACKAGE_PIN E3 IOSTANDARD LVCMOS33 } [get_ports { w_clk }];  
create_clock -add -name sys_clk -period 10.00 [get_ports { w_clk }];
```


Slice and SLICEL

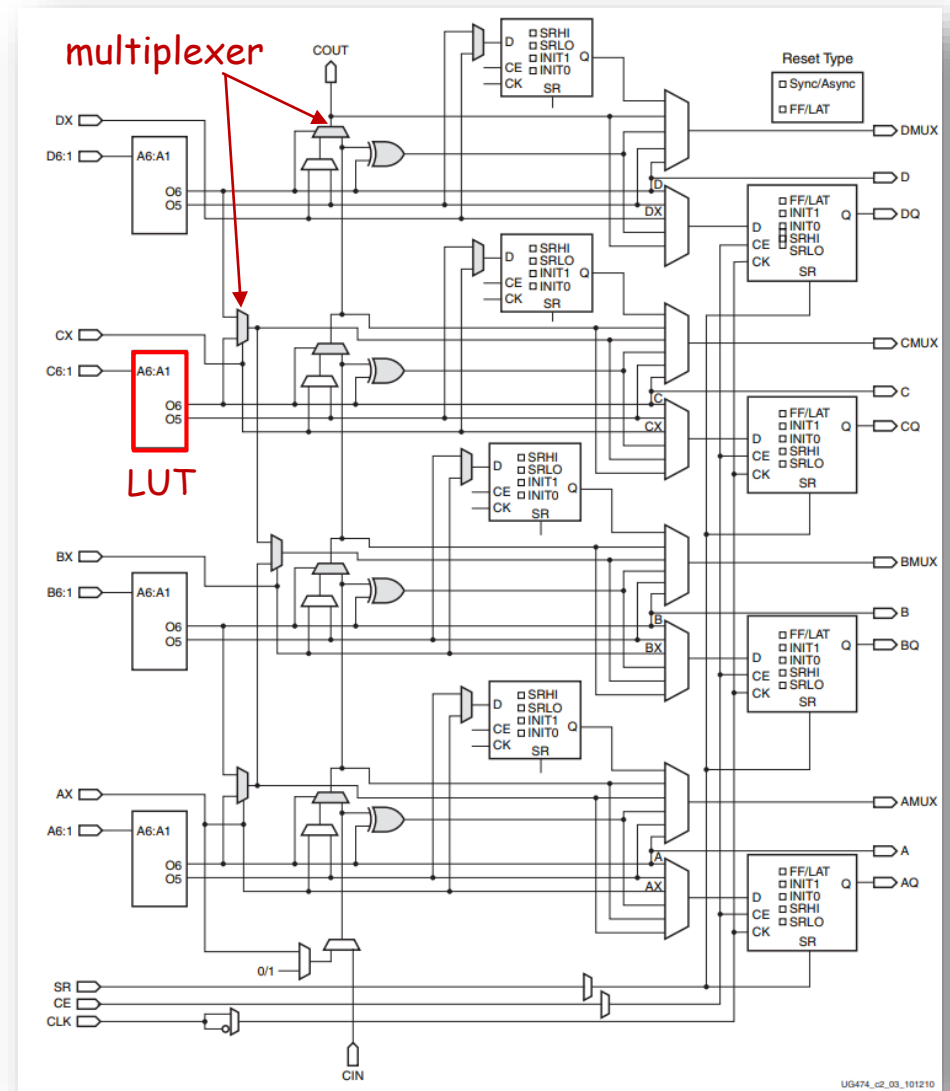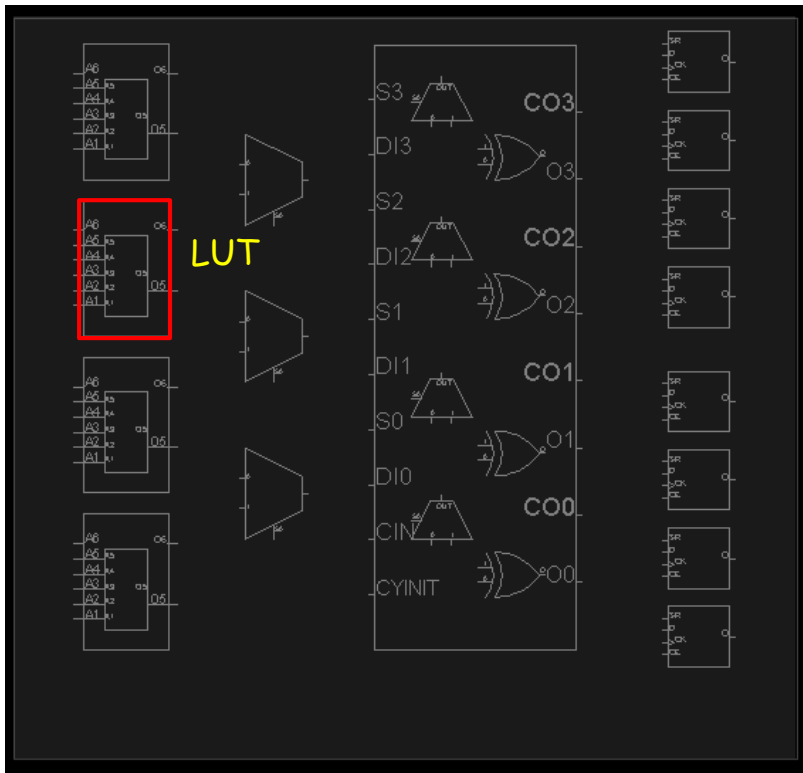- There are two types of slices. They are **SLICEL** and **SLICEM**.
- Each slice has **4 LUTs** and **8 FFs**.




CLB (Configurable Logic Block) and Slice

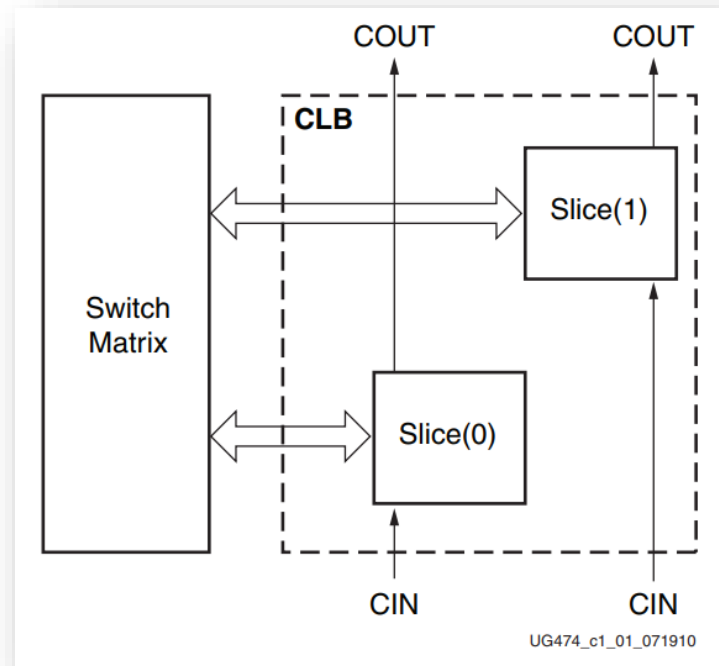- Each **CLB** has **two slices**
 - There are two types of slices. They are **SLICEL** and **SLICEM**.
 - Approximately two-thirds of the slices are **SLICEL** logic slices and the rest are **SLICEM**, which can also use their LUTs as distributed 64-bit RAM or as 32-bit shift registers (SRL32) or as two SRL16s.




FPGA (Field Programmable Gate Array)

 - Artix-7 FPGA (xc7a35tcsg324-1L)
 - 2,600 CLB = 5,200 slices




xc7a35tcsg324-1L FPGA die

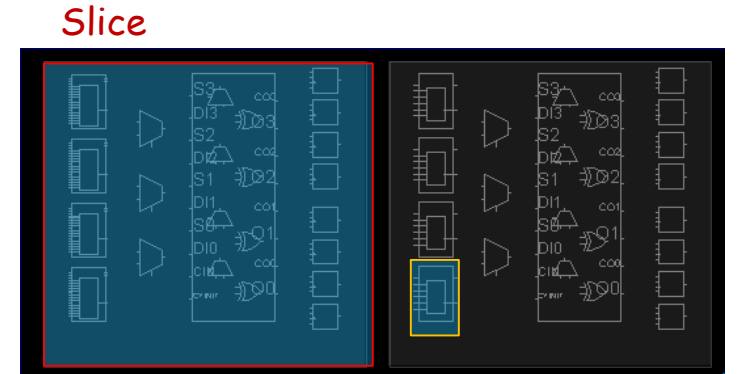

Slice

LUT (Lookup Table)

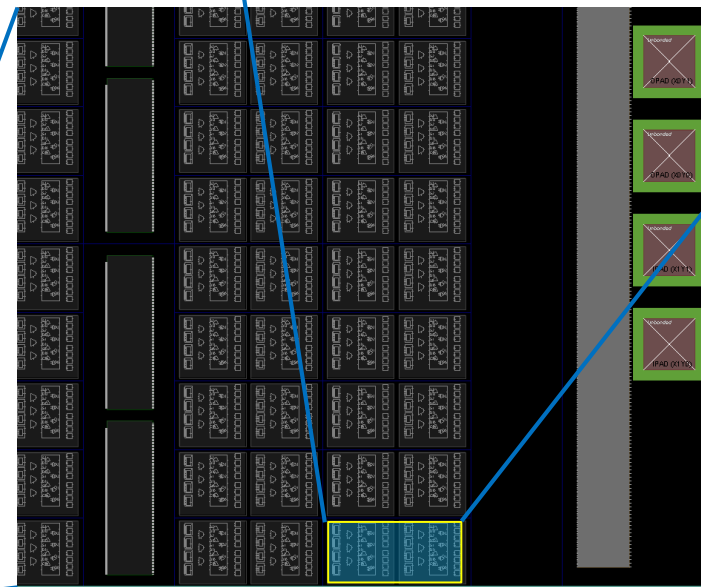

CLB (Configurable Logic Block)



Xilinx 7 Series Configuration Logic Block (CLB)

7 Series FPGAs Configurable Logic Block

User Guide

Slices = SLICEL + SLICEM
Distributed RAM (bit) = SLICEM × 256
Flip-Flops = LUTs × 2


Table 1-2: Artix-7 FPGA CLB Resources

Device	Slices ⁽¹⁾	SLICEL	SLICEM	6-input LUTs	Distributed RAM (Kb)	Shift Register (Kb)	Flip-Flops
7A12T	2,000 ⁽²⁾	1,316	684	8,000	171	86	16,000
7A15T	2,600 ⁽²⁾	1,800	800	10,400	200	100	20,800
7A25T	3,650	2,400	1,250	14,600	313	156	29,200
7A35T	5,200 ⁽²⁾	3,600	1,600	20,800	400	200	41,600
7A50T	8,150	5,750	2,400	32,600	600	300	65,200
7A75T	11,800 ⁽²⁾	8,232	3,568	47,200	892	446	94,400
7A100T	15,850	11,100	4,750	63,400	1,188	594	126,800
7A200T	33,650	22,100	11,550	134,600	2,888	1,444	269,200


UG474 (v1.8) September 27, 2016

Artix-7 Architecture Overview

 - CLB (Configurable Logic Block)
- BRAM (Block RAM, embedded memory)
- DSP (Digital Signal Processing)
- CMT (Clock Management Tile)
- Routing fabric




DSP Slice

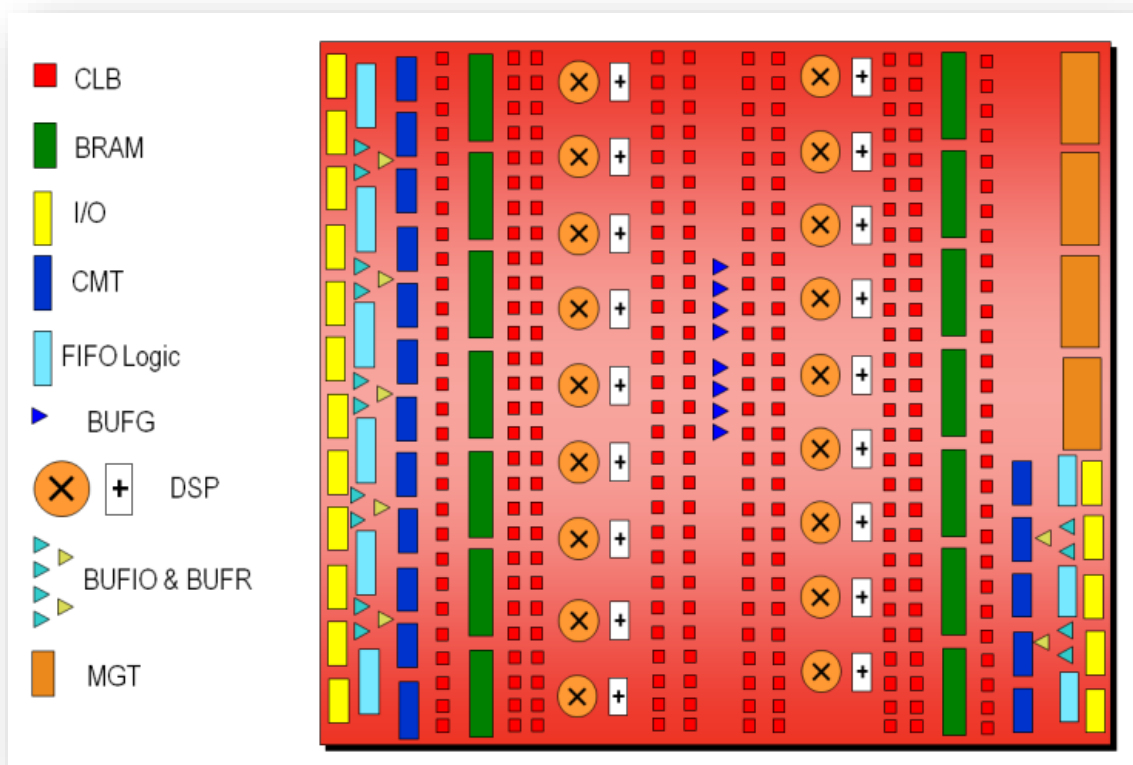

FPGA Design Flow

 - IP Integrator
- Simulation
- RTL Analysis
- **Synthesis**
 - Logic Synthesis (論理合成), ネットリストの生成
- **Implementation**
 - Place and Route (配置・配線)
- **Program and Debug**
 - Bitstream generation
 - Program



Example Synthesis Result

- ▼ SYNTHESIS
 - ▶ Run Synthesis
 - ▼ Open Synthesized Design
 - Constraints Wizard
 - Edit Timing Constraints
 - Set Up Debug
 - Report Timing Summary
 - Report Clock Networks
 - Report Clock Interaction
 - Report Methodology
 - Report DRC
 - Report Noise
 - Report Utilization
 - Report Power
 - Schematic

code090.v

```

module m_main (w_clk, w_led);
  input wire w_clk;
  output wire [3:0] w_led;


  reg [3:0] r_out = 0;
  always@(posedge w_clk) r_out <= r_out + 1;
  assign w_led = r_out;
endmodule
    
```

■ r_out[0]_i_1

I0	O=!I0
0	1
1	0


■ r_out[1]_i_1

I1	I0	O=I0 & !I1 + !I0 & I1
0	0	0
0	1	1
1	0	1
1	1	0

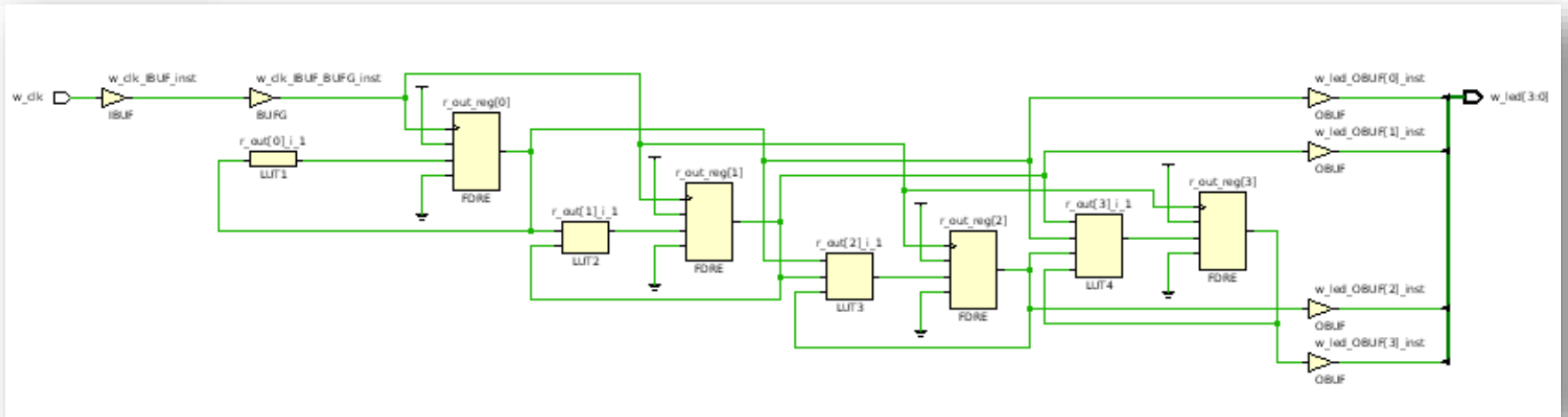

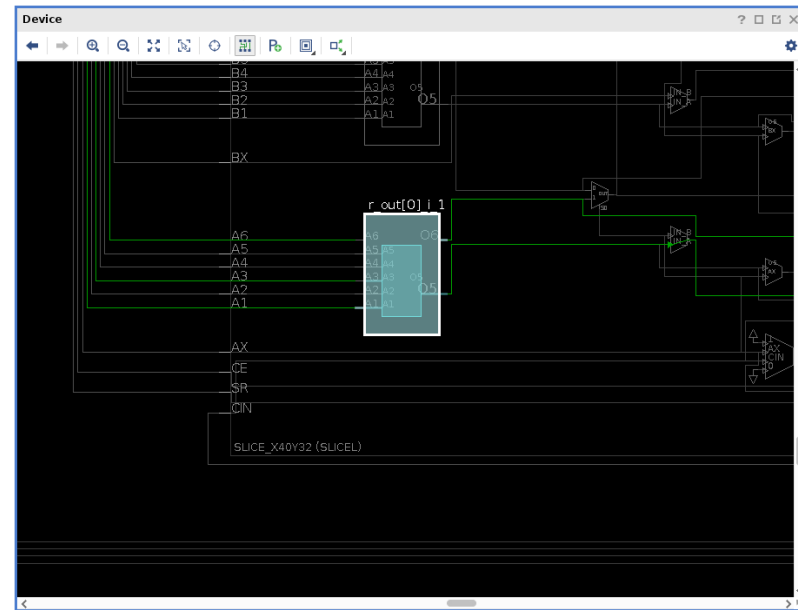Example Implementation Result

IMPLEMENTATION
 ▶ Run Implementation
 ▼ Open Implemented Design
 Constraints Wizard
 Edit Timing Constraints
 ⌚ Report Timing Summary
 Report Clock Networks
 Report Clock Interaction
 📄 Report Methodology
 Report DRC
 Report Noise
 Report Utilization
 🦋 Report Power
 🔍 Schematic



Cell Properties x Clock Regions

r_out[0]_i_1


I0	O=I0
0	1
1	0

Edit LUT Equation...

erties Power Nets Cell Pins Truth Table


r_out[1]_i_1

I1	I0	O=I0 & !I1 + !I0 & I1
0	0	0
0	1	1
1	0	1
1	1	0

 

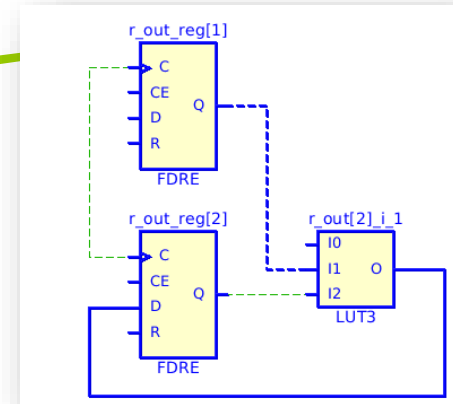Example Implementation Result

- ▼ IMPLEMENTATION
 - ▶ Run Implementation
 - ▼ Open Implemented Design
 - Constraints Wizard
 - Edit Timing Constraints
 - Report Timing Summary**
 - Report Clock Networks
 - Report Clock Interaction
 - Report Methodology
 - Report DRC
 - Report Noise
 - Report Utilization
 - Report Power
 - Schematic



◀ Design Timing Summary

Setup	Hold
Worst Negative Slack (WNS): 6.674 ns	Worst Hold Slack (WHS): 0.465 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 4	Total Number of Endpoints: 4

All user specified timing constraints are met.


🔍 - 🏠 📏 ● Intra-Clock Paths - sys_clk - Setup

Name	Slack ^{^1}	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement
Path 1	6.674	1	1	4	r_out_reg[1]/C	r_out_reg[2]/D	3.290	0.718	2.572	10.0
Path 2	6.694	1	1	4	r_out_reg[1]/C	r_out_reg[3]/D	3.316	0.744	2.572	10.0
Path 3	8.156	1	1	4	r_out_reg[1]/C	r_out_reg[1]/D	1.884	0.746	1.138	10.0
Path 4	8.172	1	1	5	r_out_reg[0]/C	r_out_reg[0]/D	1.822	0.580	1.242	10.0

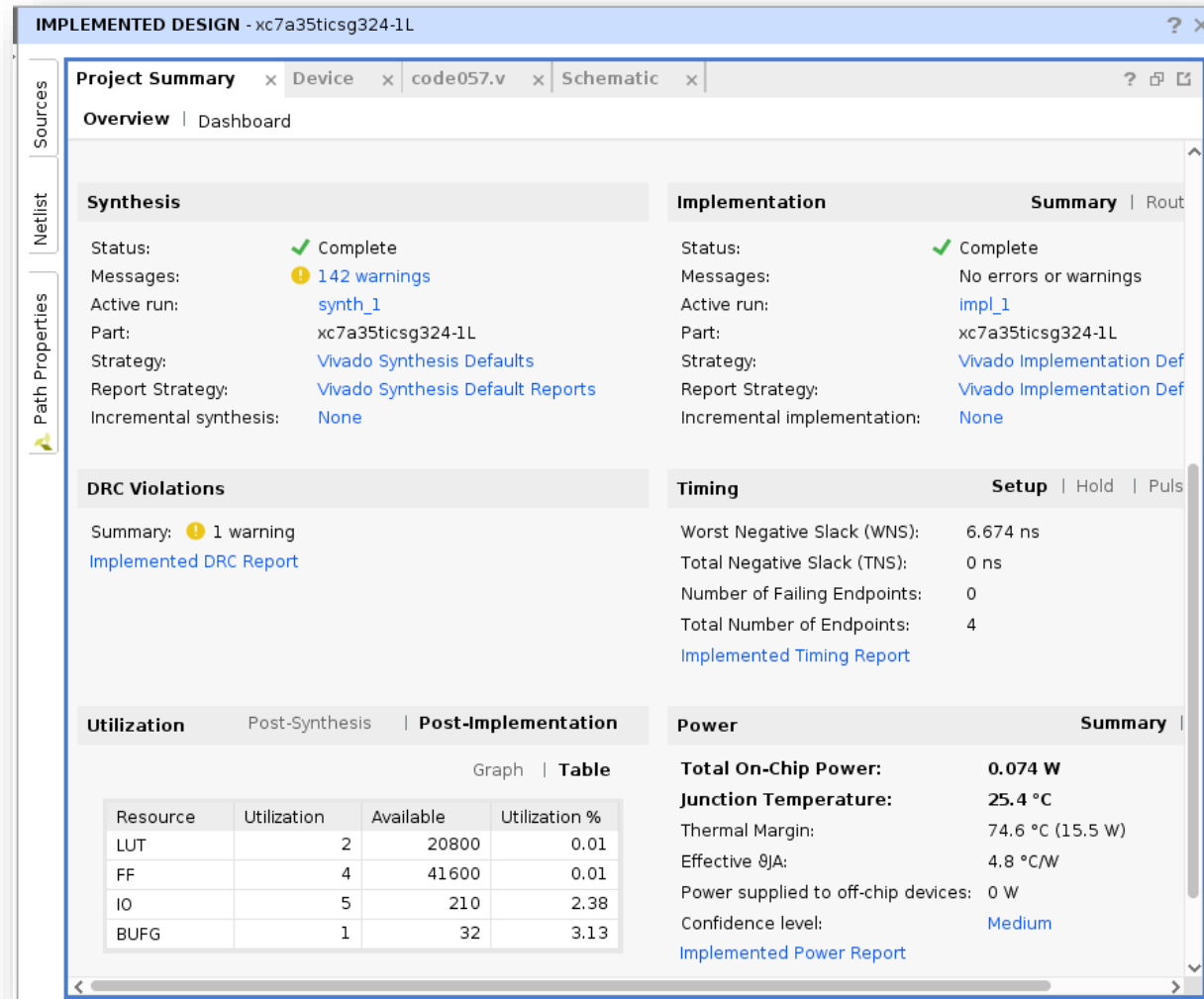Example Implementation Result

- Project Summary Window

- This window is useful to check the synthesis and implementation result at a glance.



The screenshot displays the 'Project Summary' window for an implemented design. The window is divided into several sections: Synthesis, Implementation, DRC Violations, Timing, Utilization, and Power. The Synthesis and Implementation sections both show a 'Complete' status with green checkmarks. The DRC Violations section shows 1 warning. The Timing section shows various slack and endpoint metrics. The Utilization section includes a table showing resource usage. The Power section shows total on-chip power and junction temperature.

Synthesis

Status: ✔ Complete
Messages: ! 142 warnings
Active run: synth_1
Part: xc7a35ticsg324-1L
Strategy: Vivado Synthesis Defaults
Report Strategy: Vivado Synthesis Default Reports
Incremental synthesis: None

Implementation

Status: ✔ Complete
Messages: No errors or warnings
Active run: impl_1
Part: xc7a35ticsg324-1L
Strategy: Vivado Implementation Def
Report Strategy: Vivado Implementation Def
Incremental implementation: None

DRC Violations

Summary: ! 1 warning
[Implemented DRC Report](#)

Timing

Worst Negative Slack (WNS): 6.674 ns
Total Negative Slack (TNS): 0 ns
Number of Failing Endpoints: 0
Total Number of Endpoints: 4
[Implemented Timing Report](#)

Utilization

Resource	Utilization	Available	Utilization %
LUT	2	20800	0.01
FF	4	41600	0.01
IO	5	210	2.38
BUFG	1	32	3.13


Power

Total On-Chip Power: 0.074 W
Junction Temperature: 25.4 °C
Thermal Margin: 74.6 °C (15.5 W)
Effective θJA: 4.8 °C/W
Power supplied to off-chip devices: 0 W
Confidence level: Medium
[Implemented Power Report](#)




Distributed RAM としても利用できる LUT

 - Reconfigurable Logic
 - 3-input LUT has 8 configuration registers
 - 6-input LUT for Artix-7 FPGA




Truth table

a	b	cin	s
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

3-input LUT structure


 


6-input LUT for Artix-7 FPGA



Slice, SLICEL and SLICEM

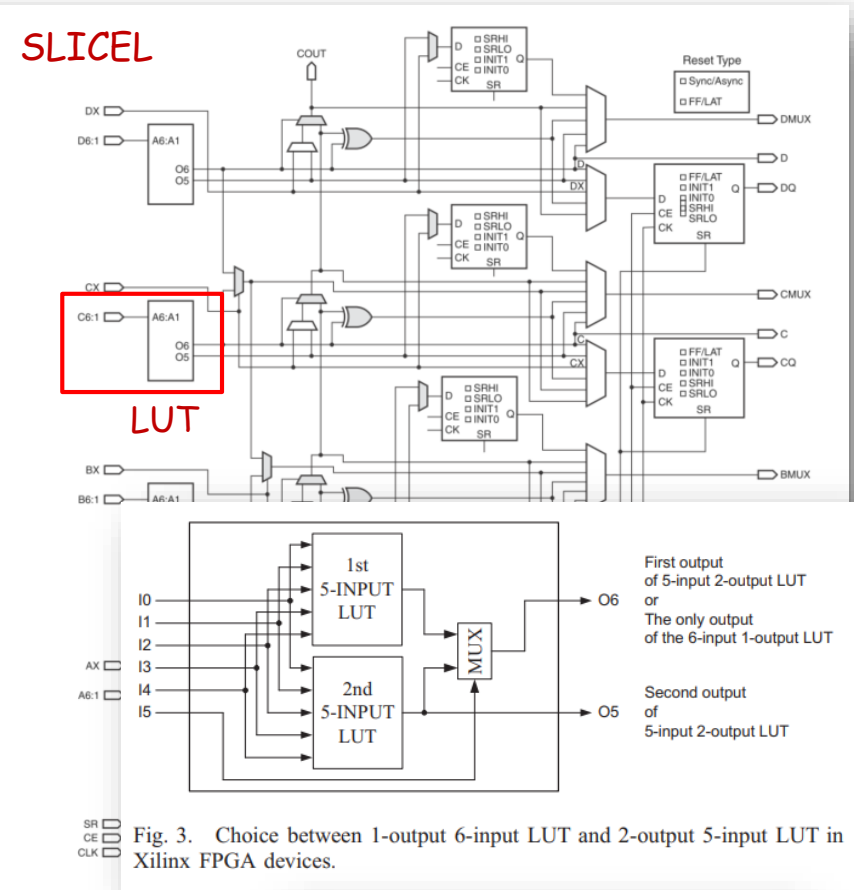 Approximately two-thirds of the slices are SLICEL logic slices and the rest are SLICEM, which can also use their LUTs as distributed 64-bit RAM (LUTRAM) or as 32-bit shift registers (SRL32) or as two SRL16s.



On Area-Efficient Implementation of Data Delays in 7 Series Xilinx FPGAs

Marek Parfieniuk
 Department of Digital Media and Computer Graphics
 Białystok University of Technology
 Wiejska 45A, 15-351 Białystok, Poland
 Email: m.parfieniuk@pb.edu.pl

Sang Yoon Park
 Department of Electronic Engineering and MPEES-ARC
 Myongji University
 Yongin 449-728, Korea
 Email: sypark@mjnu.ac.kr

Distributed RAM (分散メモリ)

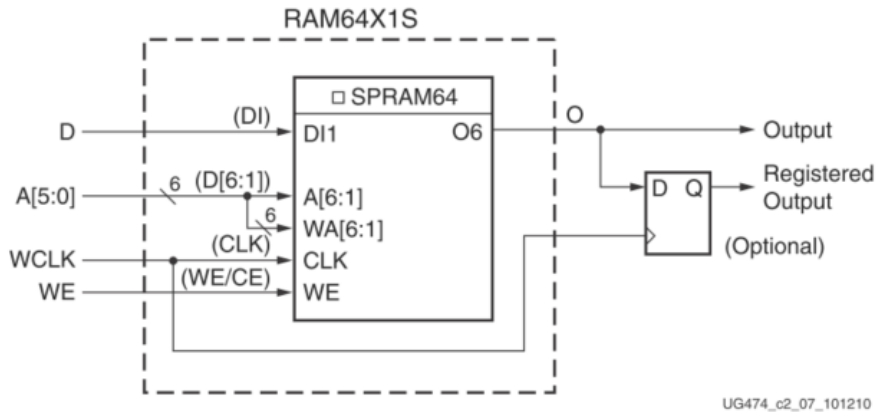


Figure 2-8: 64 X 1 Single Port Distributed RAM (RAM64X1S)

```

module m_RAM64X1S (clk, a, d, we, dout);
  input wire clk;      // clock signal
  input wire [5:0] a;  // address
  input wire d, we;    // data_in, write_enable
  output wire dout;    // data_out

  reg [0:0] mem [0:63];
  assign dout = mem[a];
  always @(posedge clk) if(we) mem[a] <= d;
endmodule
    
```

LUTRAM = 1


Table 2-3: Distributed RAM Configuration

RAM	Description	Primitive	Number of LUTs
32 x 1S	Single port	RAM32X1S	1
32 x 1D	Dual port	RAM32X1D	2
32 x 2Q	Quad port	RAM32M	4
32 x 6SDP	Simple dual port	RAM32M	4
64 x 1S	Single port	RAM64X1S	1
64 x 1D	Dual port	RAM64X1D	2
64 x 1Q	Quad port	RAM64M	4
64 x 3SDP	Simple dual port	RAM64M	4
128 x 1S	Single port	RAM128X1S	2
128 x 1D	Dual port	RAM128X1D	4
256 x 1S	Single port	RAM256X1S	4

- Single port
 - Common address port for synchronous writes and asynchronous reads
 - Read and write addresses share the same address bus



Distributed RAM (分散メモリ)

 

UG474_c2_06_070914

Figure 2-6: 32 X 2 Quad Port Distributed RAM (RAM32M)


Table 2-3: Distributed RAM Configuration

RAM	Description	Primitive	Number of LUTs
32 x 1S	Single port	RAM32X1S	1
32 x 1D	Dual port	RAM32X1D	2
32 x 2Q	Quad port	RAM32M	4
32 x 6SDP	Simple dual port	RAM32M	4
64 x 1S	Single port	RAM64X1S	1
64 x 1D	Dual port	RAM64X1D	2
64 x 1Q	Quad port	RAM64M	4
64 x 3SDP	Simple dual port	RAM64M	4
128 x 1S	Single port	RAM128X1S	2
128 x 1D	Dual port	RAM128X1D	4
256 x 1S	Single port	RAM256X1S	4

- Quad port
 - One port for synchronous writes and asynchronous reads
 - Three ports for asynchronous reads



Distributed RAM (分散メモリ)

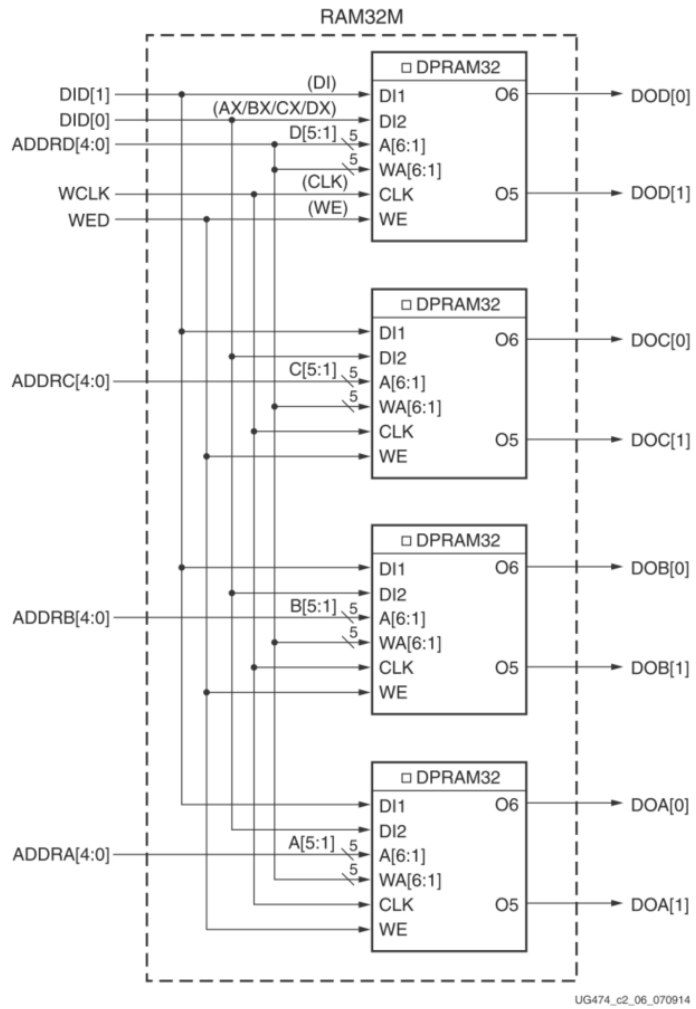

```

module m_RAM32M_Q (clk, a1, a2, a3, a4, d, we, dout1, dout2, dout3, dout4);
    input wire clk;
    input wire [4:0] a1, a2, a3, a4;
    input wire [1:0] d;
    input wire we;
    output wire [1:0] dout1, dout2, dout3, dout4;

    reg [1:0] mem [0:31];
    assign dout1 = mem[a1];
    assign dout2 = mem[a2];
    assign dout3 = mem[a3];
    assign dout4 = mem[a4];
    always @(posedge clk) if(we) mem[a1] <= d;
endmodule
    
```

Failed Routes	LUT	FF	BRAM	URAM	DSP
	4	0	0.0	0	0
	0	4	0.0	0	0

LUTRAM = 4

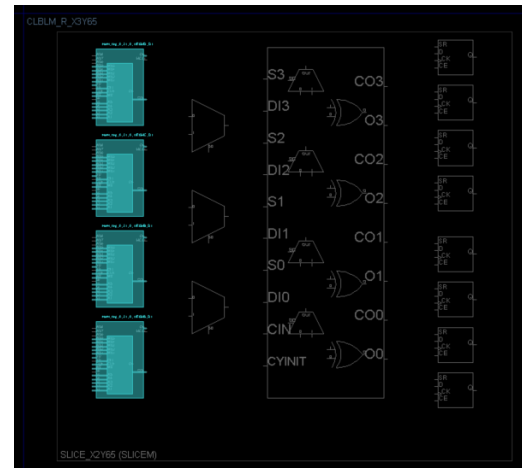


Figure 2-6: 32 X 2 Quad Port Distributed RAM (RAM32M)



Register file design of RISC-V soft processors



32x32 (32regs-32bit) single port register file

```
module m_RegFile_S (clk, a, d, we, dout);
  input wire clk;
  input wire [4:0] a;
  input wire [31:0] d;
  input wire we;
  output wire [31:0] dout;

  reg [31:0] mem [0:31];
  assign dout = mem[a];
  always @(posedge clk) if(we) mem[a] <= d;
endmodule
```

LUTRAM = 32

32x32 (32regs-32bit) dual port register file

```
module m_RegFile_D (clk, a1, a2, d, we, dout1, dout2);
  input wire clk;
  input wire [4:0] a1, a2;
  input wire [31:0] d;
  input wire we;
  output wire [31:0] dout1, dout2;

  reg [31:0] mem [0:31];
  assign dout1 = mem[a1];
  assign dout2 = mem[a2];
  always @(posedge clk) if(we) mem[a1] <= d;
endmodule
```


Resource	Utilization	Available	Utilization %
LUT	32	63400	0.05
LUTRAM	32	19000	0.17
IO	108	210	51.43
BUFG	1	32	3.13



BRAM (Block RAM)

<https://www.acri.c.titech.ac.jp/wordpress/archives/10236>

BRAM 達人への道 (1) 構造と基本的な使い方

 

© 2021.01.21

FPGA を用いて AI のアクセラレーションのような高度な処理を行うことが当たり前の時代になりました。しかし、FPGA を利用する全てのエンジニアがそうしたアプリケーションに携わっているわけではなく、初心者、初級者レベルのエンジニアが多数おられるということも事実ではないかと思えます。

この記事では、現場レベルで使えるちょっとした工夫や考え方のヒントを紹介し、初級者のレベルアップや、現場の方々の手助けにつながればと考えています。



Configuration bitstream

- Bit vector of all configuration registers.
 - Program FPGA using a configuration chain of shift register like hardware.


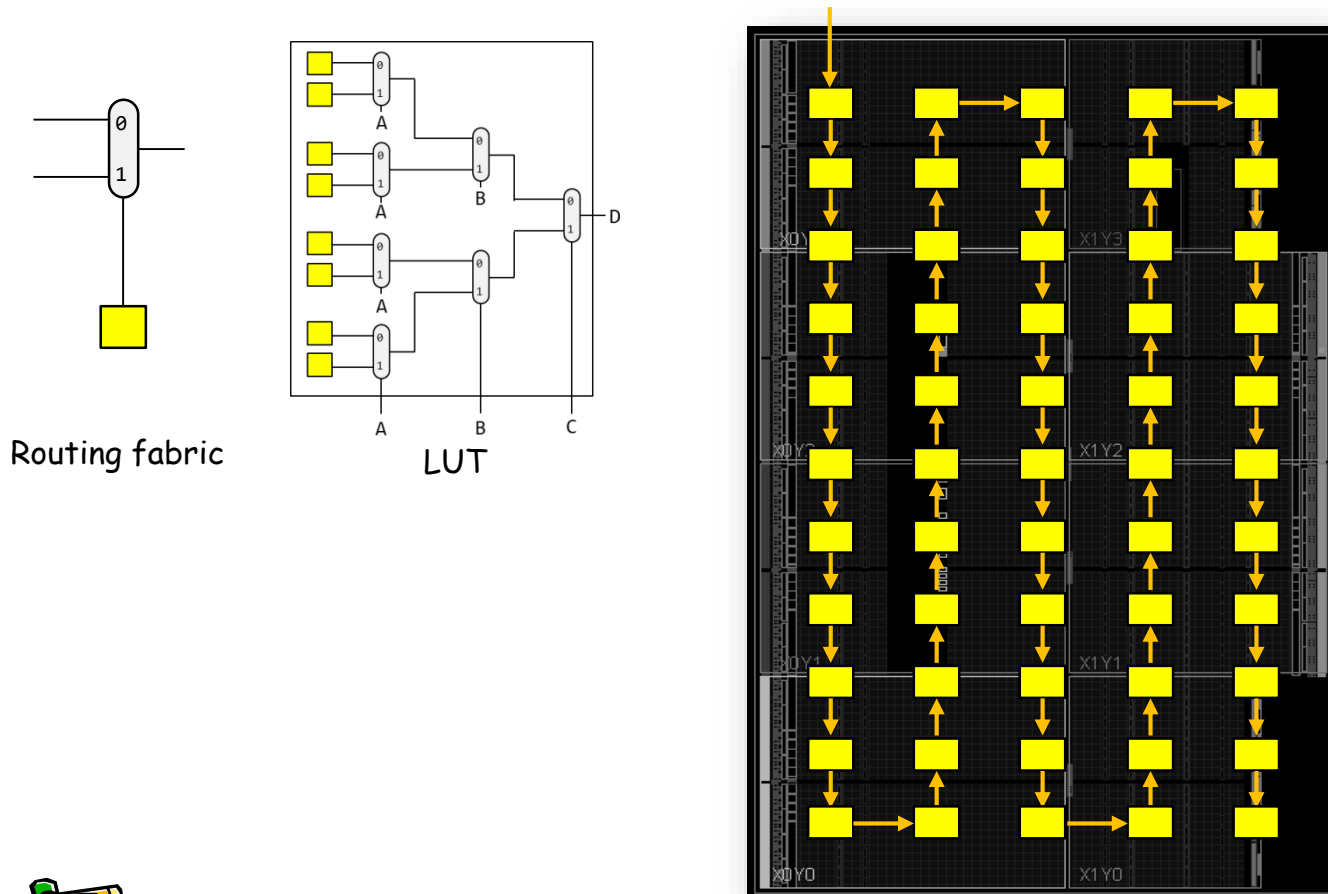


表 1-1: ビットストリームの長さ


デバイス	コンフィギュレーションビットストリームの長さ (ビット)
Artix-7 ファミリー	
7A15T	17,536,096
7A35T	17,536,096
7A50T	17,536,096
7A75T	30,606,304
7A100T	30,606,304
7A200T	77,845,216

Artix-7 Architecture Overview

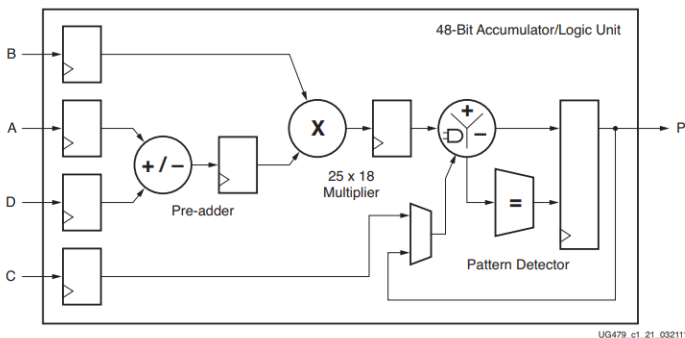- CLB (Configurable Logic Block)
- BRAM (Block RAM, embedded memory)
- DSP (Digital Signal Processing)
- CMT (Clock Management Tile)
- Routing fabric





DSP Slice

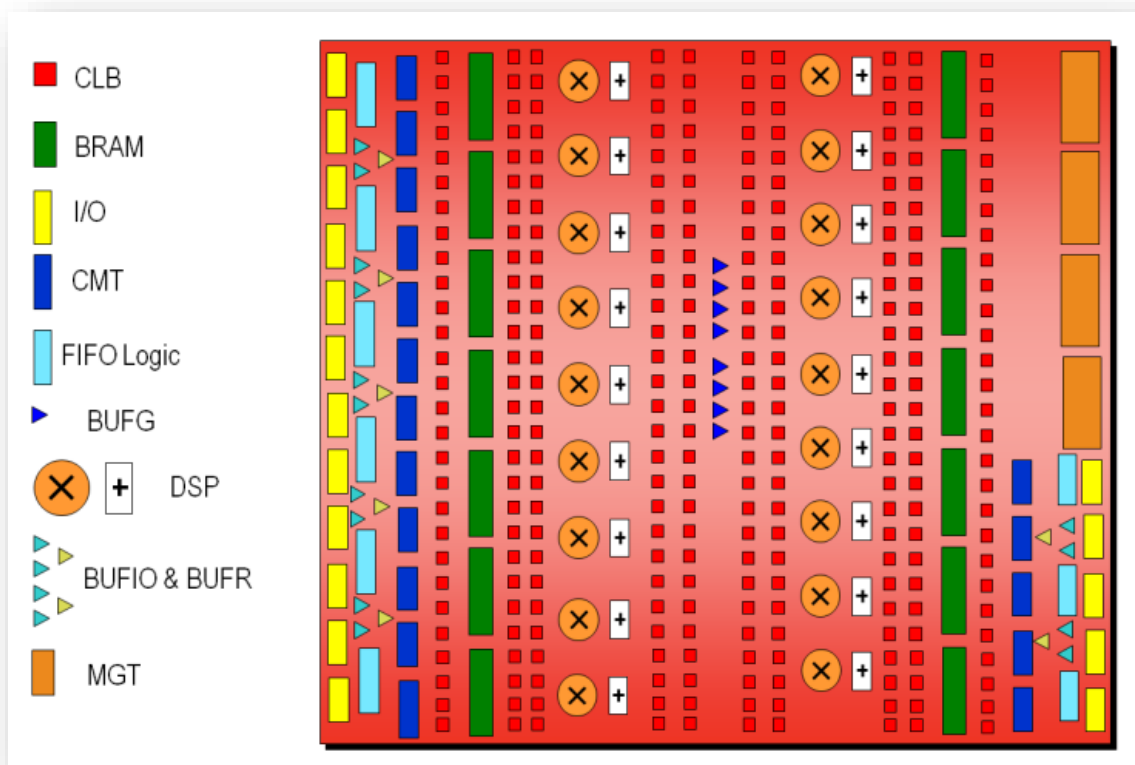

ACRiルームのデモンストレーション

  - LUT で実現される真理値表を確認する方法.
- Clocking Wizard を使って 20MHz のクロック信号を生成する方法.



Carry Chain in slice

Article Mapping Arbitrary Logic Functions onto Carry Chains in FPGAs

Raouf Senhadji-Navarro *[†] and Ignacio Garcia-Vargas [†]

Department of Computer Architecture and Technology, University of Seville, 41012 Seville, Spain; iggv@us.es

* Correspondence: raouf@us.es

† These authors contributed equally to this work.

Abstract: Current Field Programmable Gate Arrays (FPGAs) provide fast routing links and special logic to perform carry operations; however, these resources can also be used to implement non-arithmetic circuits. In this paper, a new approach for mapping logic functions onto carry chains is presented. Unlike other approaches, the proposed technique can be applied to any logic function

 
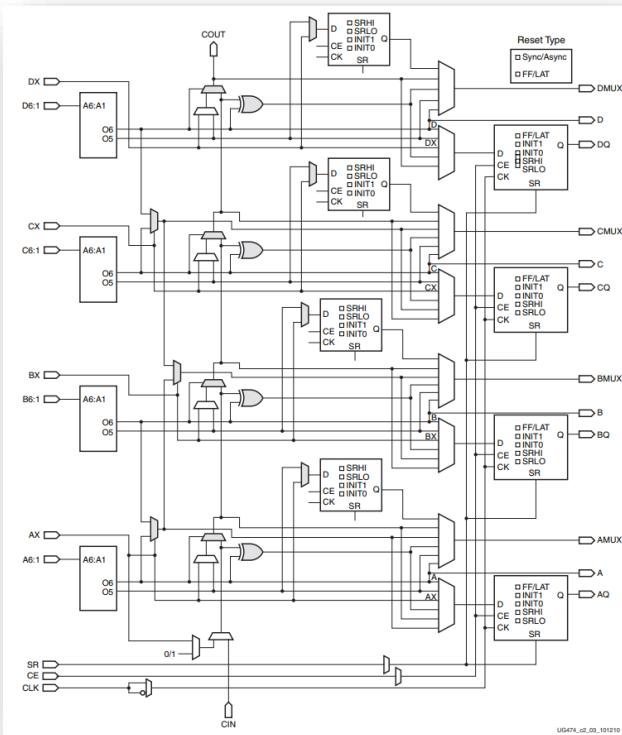


Figure 2. A 3-bit full adder implemented in a Xilinx FPGA device using carry chains.

 


Figure 3. Examples of the implementation of wide input functions using carry chains: (a) 24-input AND and (b) 24-input OR.

References

- Computer Logic Design support page
 - <https://www.arch.cs.titech.ac.jp/lecture/CLD/>
- ACRi Room
 - <https://gw.acri.c.titech.ac.jp>
- ACRi Blog
 - <https://www.acri.c.titech.ac.jp/wordpress/>
- 情報工学系計算機室
 - <http://www.csc.titech.ac.jp/>
- Xilinx Vivado Design Suite
 - <https://japan.xilinx.com/products/design-tools/vivado.html>
- Digilent Arty A7-35T
 - <https://reference.digilentinc.com/reference/programmable-logic/arty-a7/start>
- Verilog HDL
 - <https://ja.wikipedia.org/wiki/Verilog>

