

Fiscal Year 2021

Ver. 2021-12-20a

Course number: CSC.T433
School of Computing,
Graduate major in Computer Science

Advanced Computer Architecture

4. Pipelining

www.arch.cs.titech.ac.jp/lecture/ACA/
Room No.W936
Mon 14:20-16:00, Thr 14:20-16:00


Kenji Kise, Department of Computer Science
kise_at_c.titech.ac.jp



Datapath of processor supporting ADD and ADDI



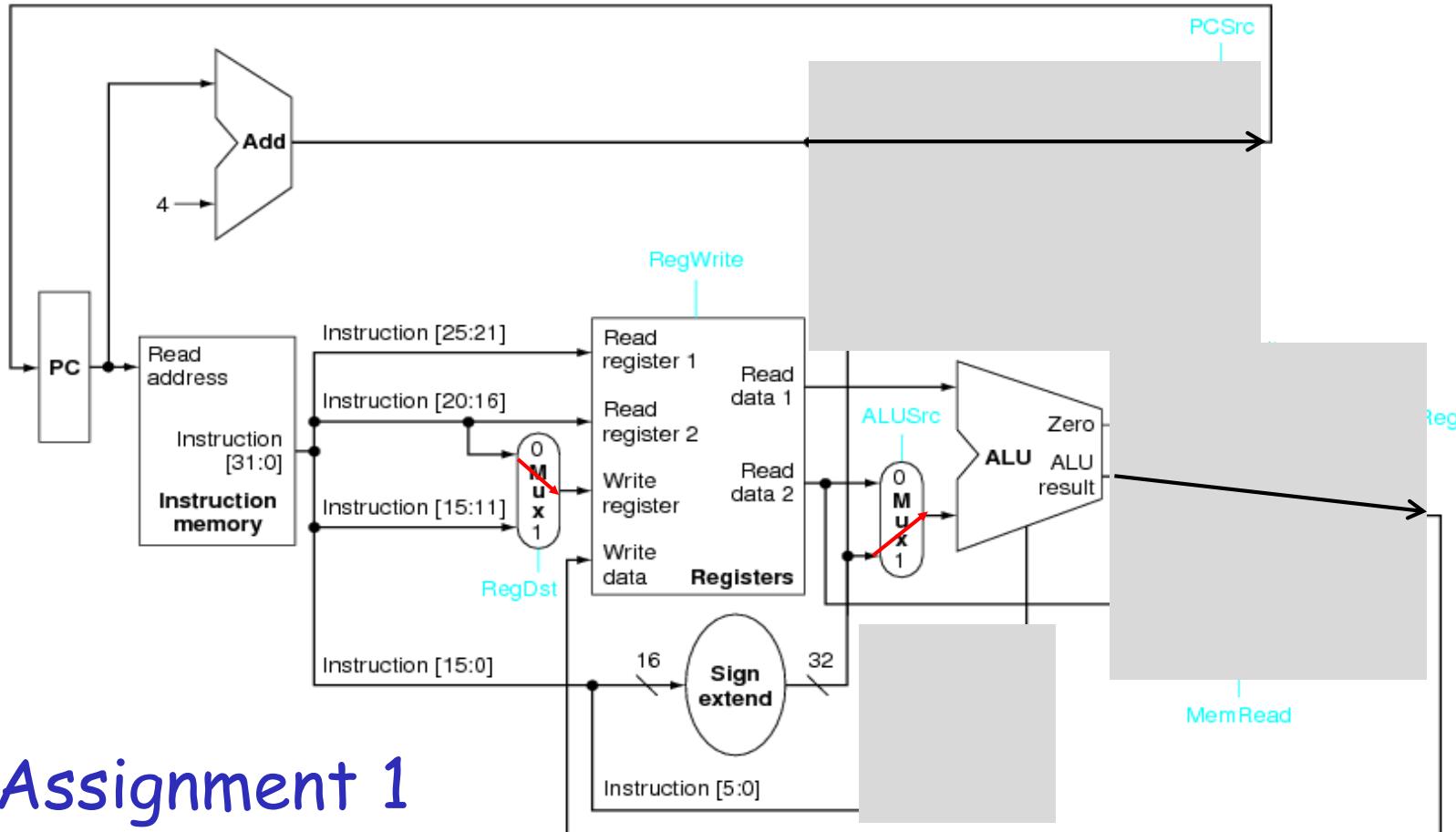
0x804 addi \$t1, \$t0, 3 [addi \$9, \$8, 3]



Datapath of processor supporting ADD, ADDI, LW, SW



0x80c sw \$t2, 8(\$t0) [sw \$10, 8(\$8)]

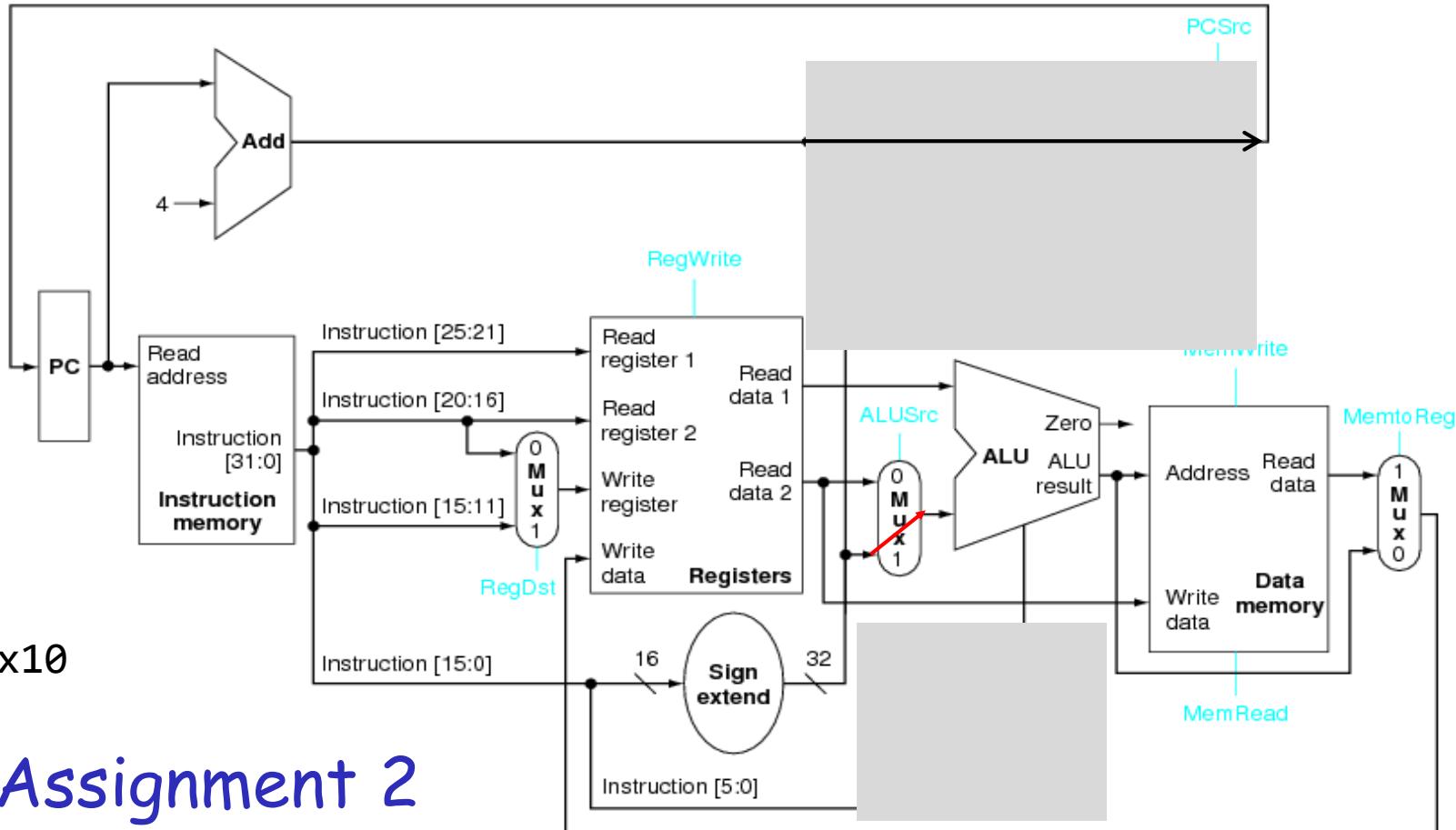

$$\$8 = 0x10$$

$$\$10 = 2$$

Assignment 2

Waveform of proc04 (Assignment 2)

cc0

cc1

add

cc2

addi

cc3


sw

cc4

lw

cc5

addi

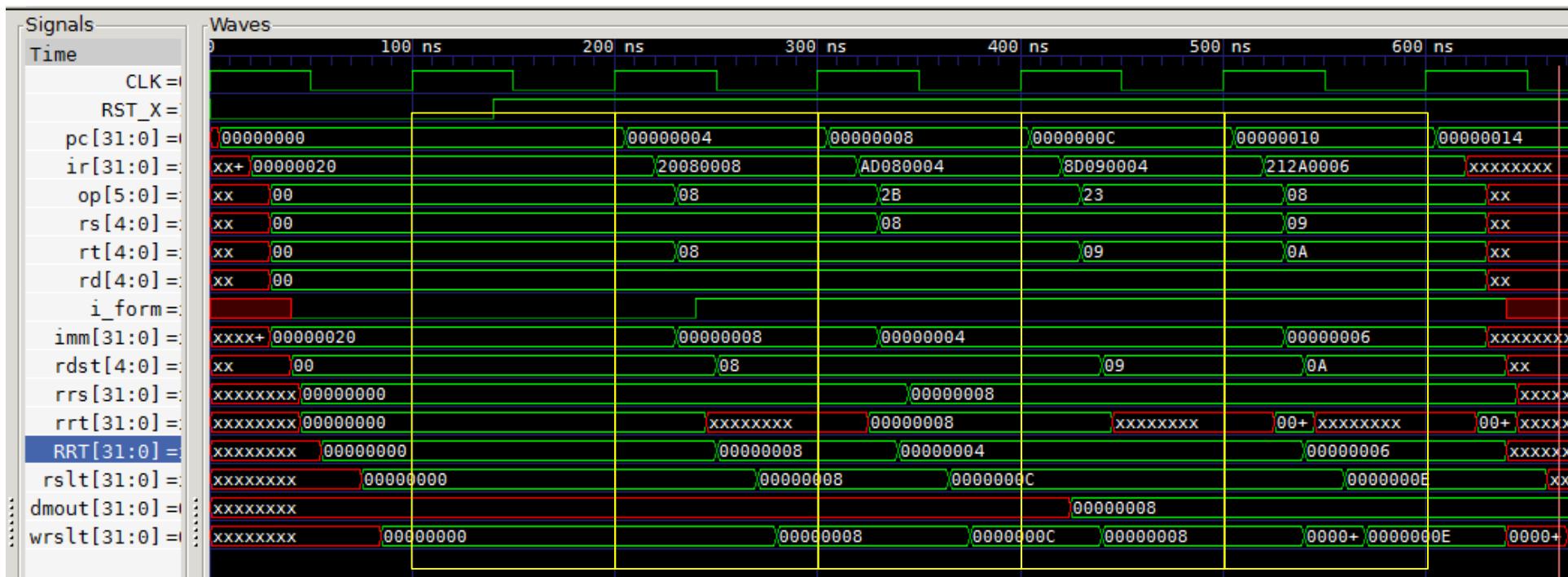

- add \$0, \$0, \$0 # NOP {6'h0, 5'd0, 5'd0, 5'd0, 5'd0, 6'h20}
- addi \$t0, \$zero, 8 # {6'h8, 5'd0, 5'd8, 16'd8} \$t0 = 8
- sw \$t0, 4(\$t0) # {6'h2b,5'd8, 5'd8, 16'd4} mem[12] = 8
- lw \$t1, 4(\$t0) # {6'h23,5'd8, 5'd9, 16'd4} \$t1 = mem[12] = 8
- addi \$t2, \$t1, 6 # {6'h8, 5'd9, 5'd10,16'd6} \$t2 = 8 + 6



MIPS Control Flow Instructions

- MIPS **conditional branch** instructions:

bne \$s0, \$s1, Lbl # go to Lbl if \$s0≠\$s1

beq \$s0, \$s1, Lbl # go to Lbl if \$s0=\$s1

- Ex: if (i==j) h = i + j;

bne \$s0, \$s1, Lbl1

add \$s3, \$s0, \$s1


Lbl1: ...

- Instruction Format (**I** format):

op	rs	rt	16 bit offset
----	----	----	---------------

 - How is the branch destination address specified?






Datapath of processor supporting ADD, ADDI, LW, SW, BNE, BEQ



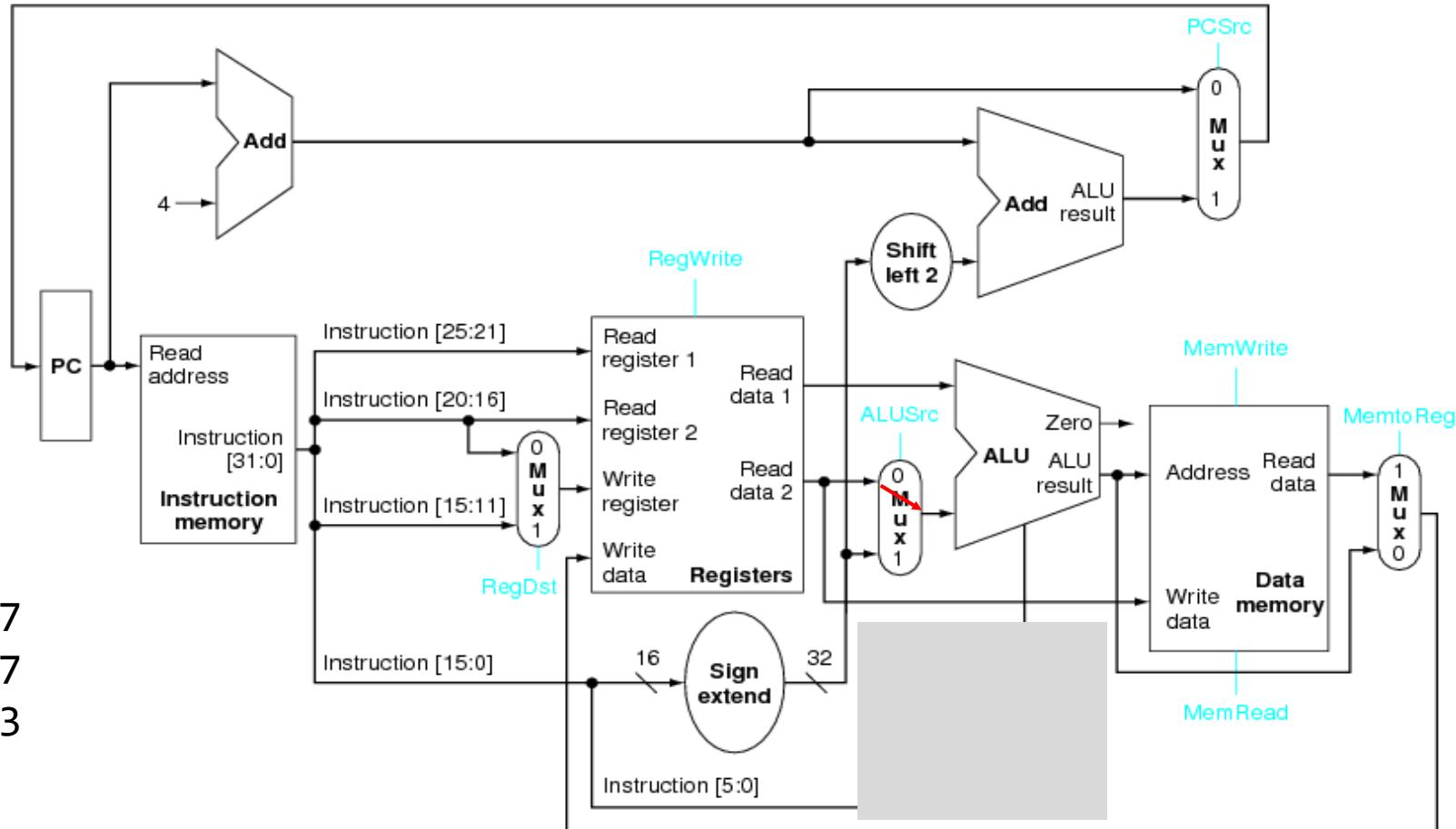0x810 beq \$t0, \$t1, Lb [beq \$8, \$9, Lb]




$$\begin{aligned} \$8 &= 7 \\ \$9 &= 7 \\ \text{imm} &= -3 \end{aligned}$$






Single-cycle implementation of processors

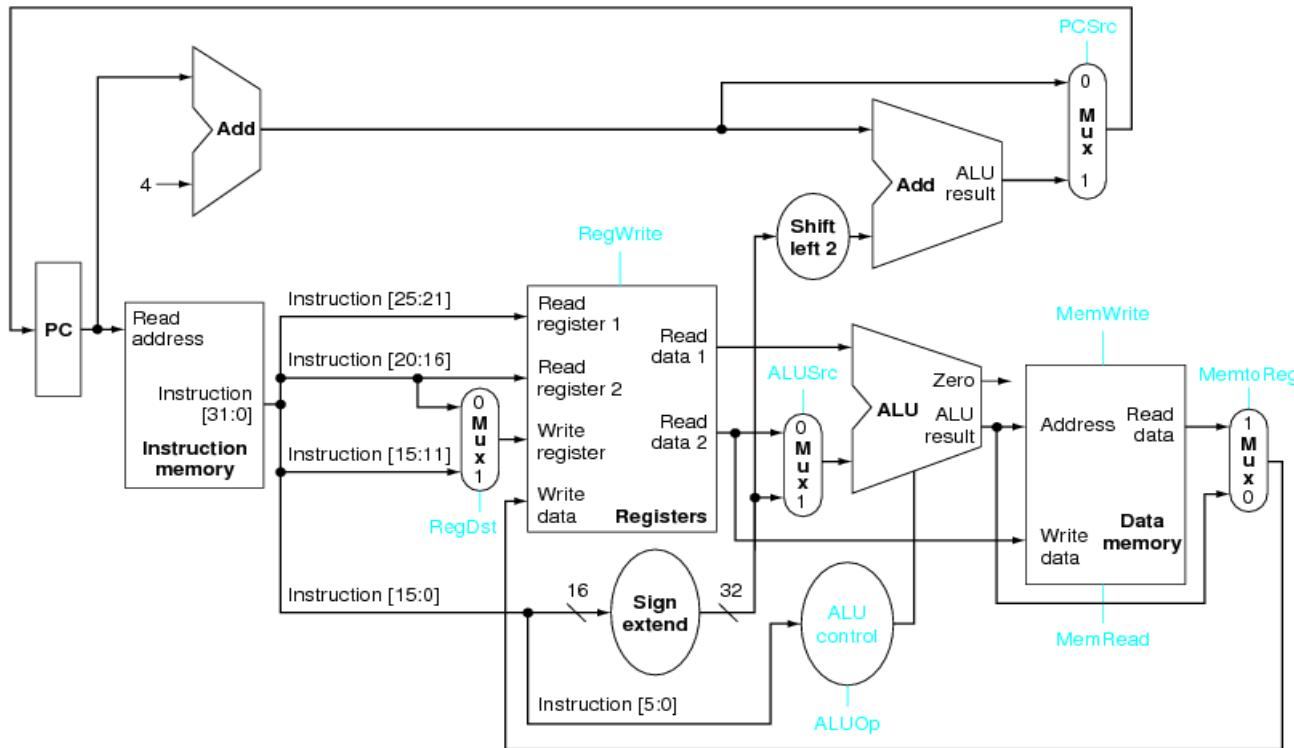- Single-cycle implementation also called **single clock cycle implementation** is the implementation in which an instruction is executed in one clock cycle. While easy to understand, it is too slow to be practical.




Single-cycle implementation of laundry

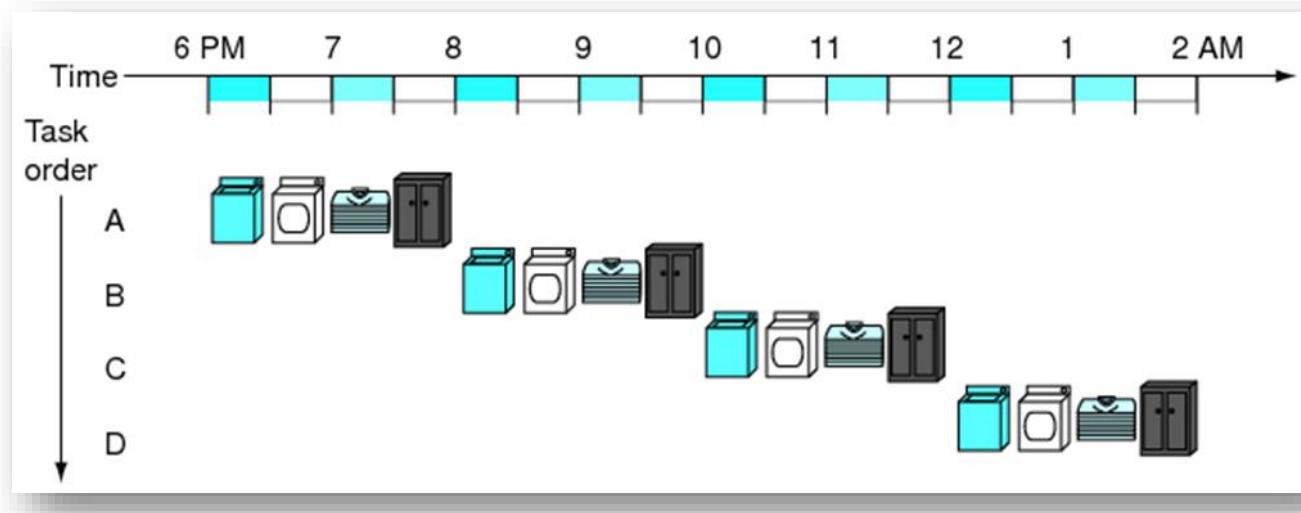- (A) Ann, (B) Brian, (C) Cathy, and (D) Don each have dirty clothes to be washed, dried, folded, and put away where each takes 30 minutes.
- Cycle time is 2 hours.
- Sequential laundry takes 8 hours for 4 loads.




Single-cycle implementation and pipelining

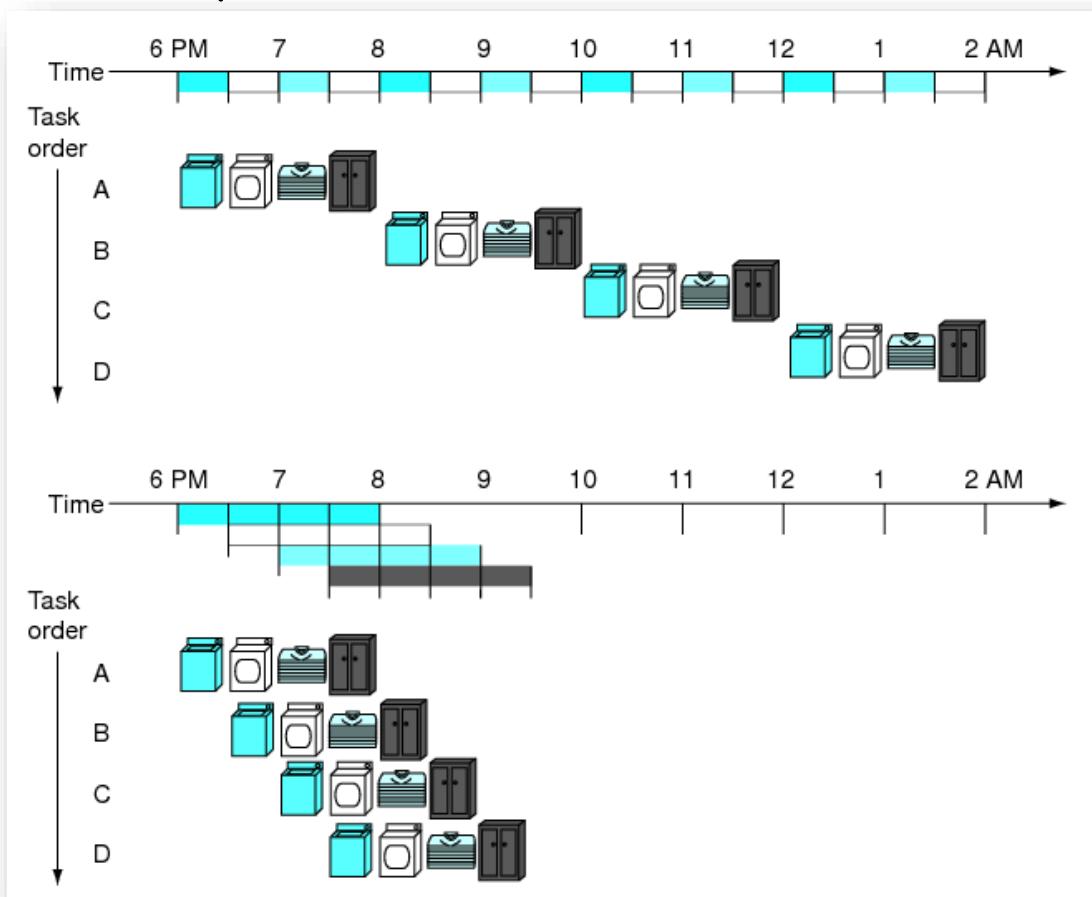- Pipelined laundry takes 3.5 hours just using the same hardware resources. Cycle time is 30 minutes.
- What is the latency of each load?




Single-cycle and pipelined processors

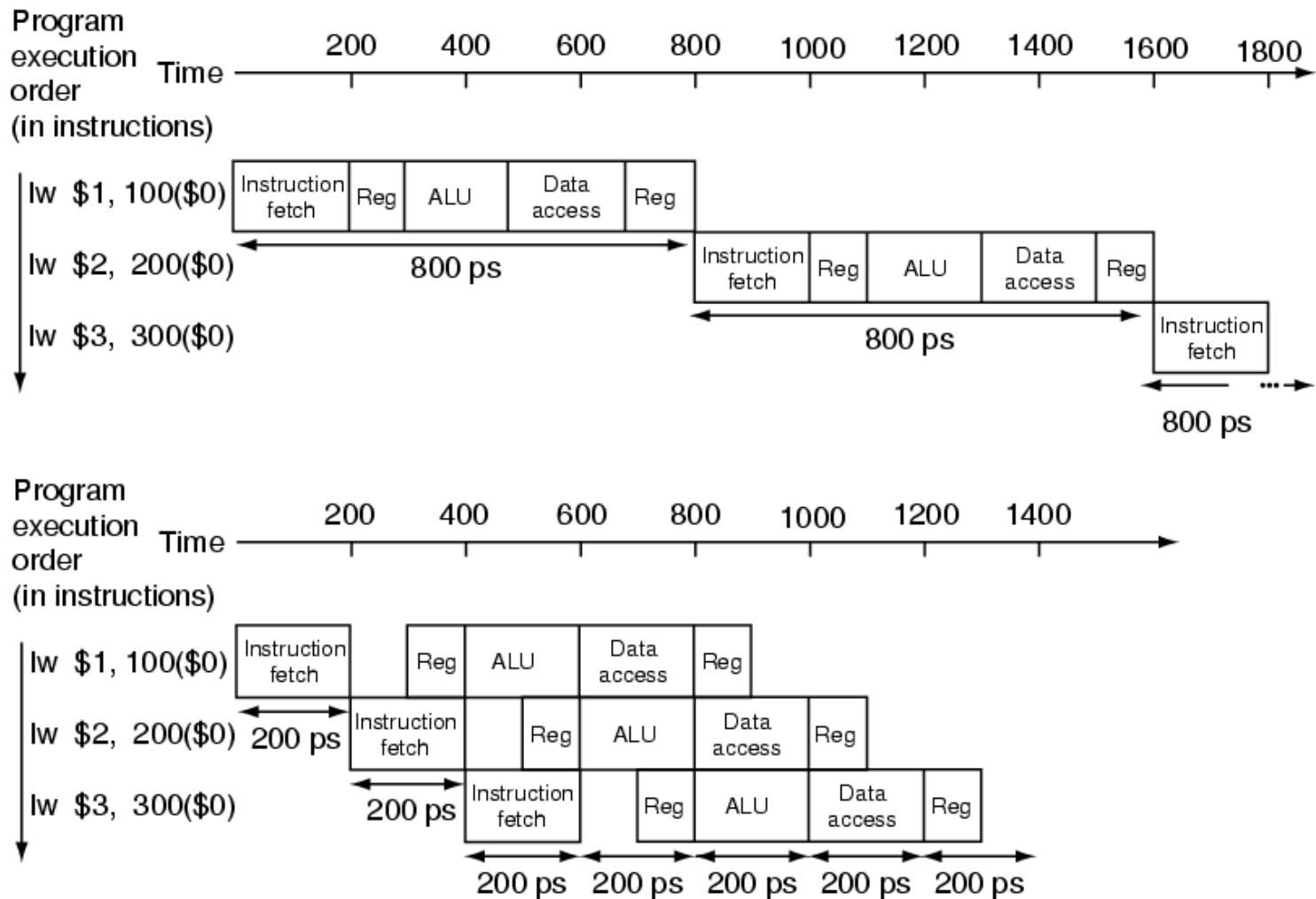


Conventional five steps (stages) of MIPS

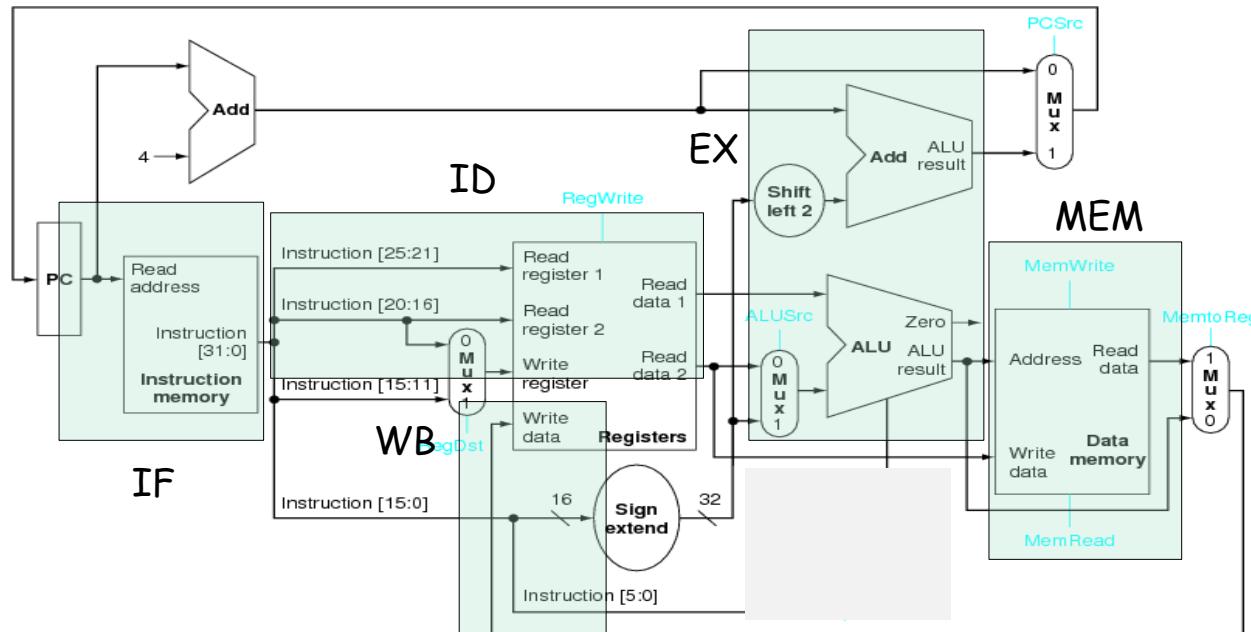
- **IF**: Instruction Fetch from instruction memory
- **ID**: Instruction Decode and operand fetch from regfile (register file)
- **EX**: EXecute operation or calculate address for load/store or calculate branch condition and target address
- **MEM (MA)**: MEMory access for load/store
- **WB**: Write result Back to regfile




Towards four stage pipelined one supporting ADD

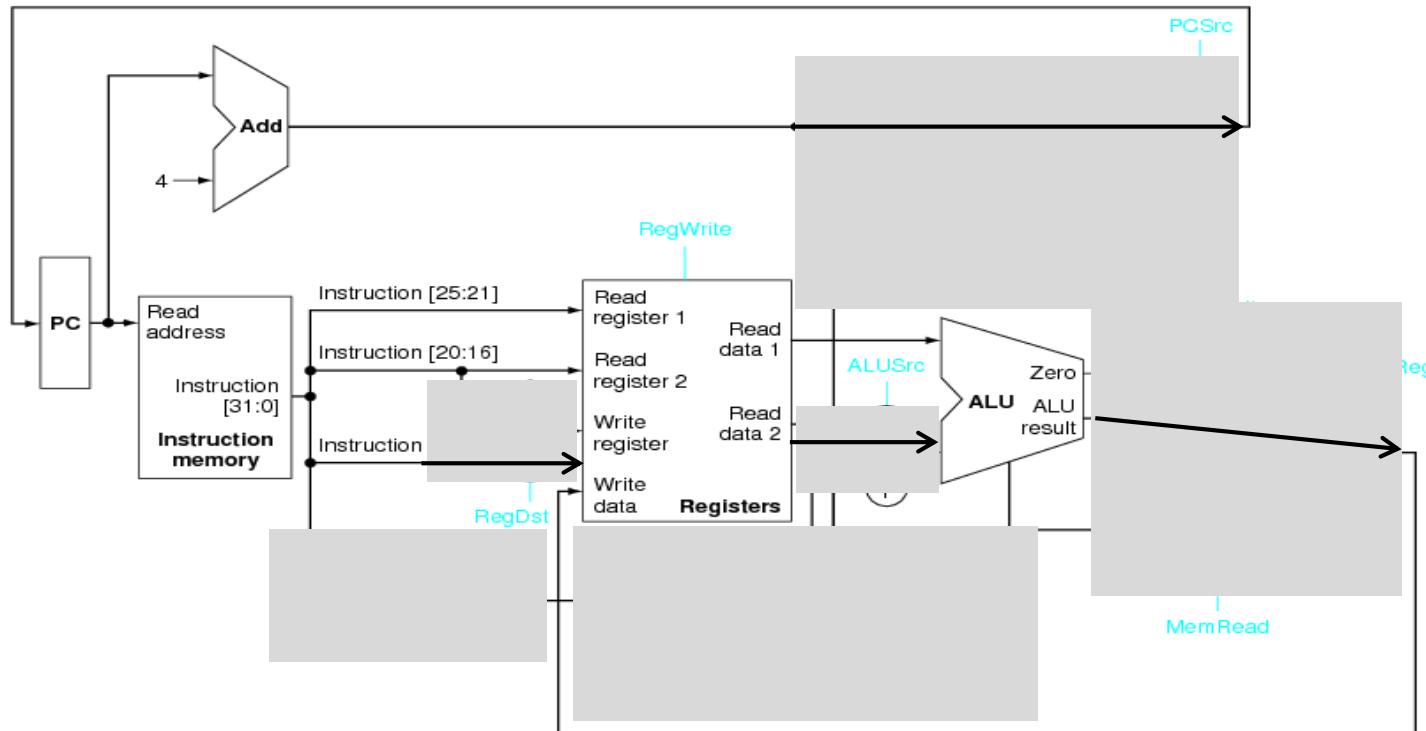- **IF**: Instruction Fetch from instruction memory
- **ID**: Instruction Decode and operand fetch from regfile
- **EX**: EXecute operation
- **WB**: Write result Back to regfile



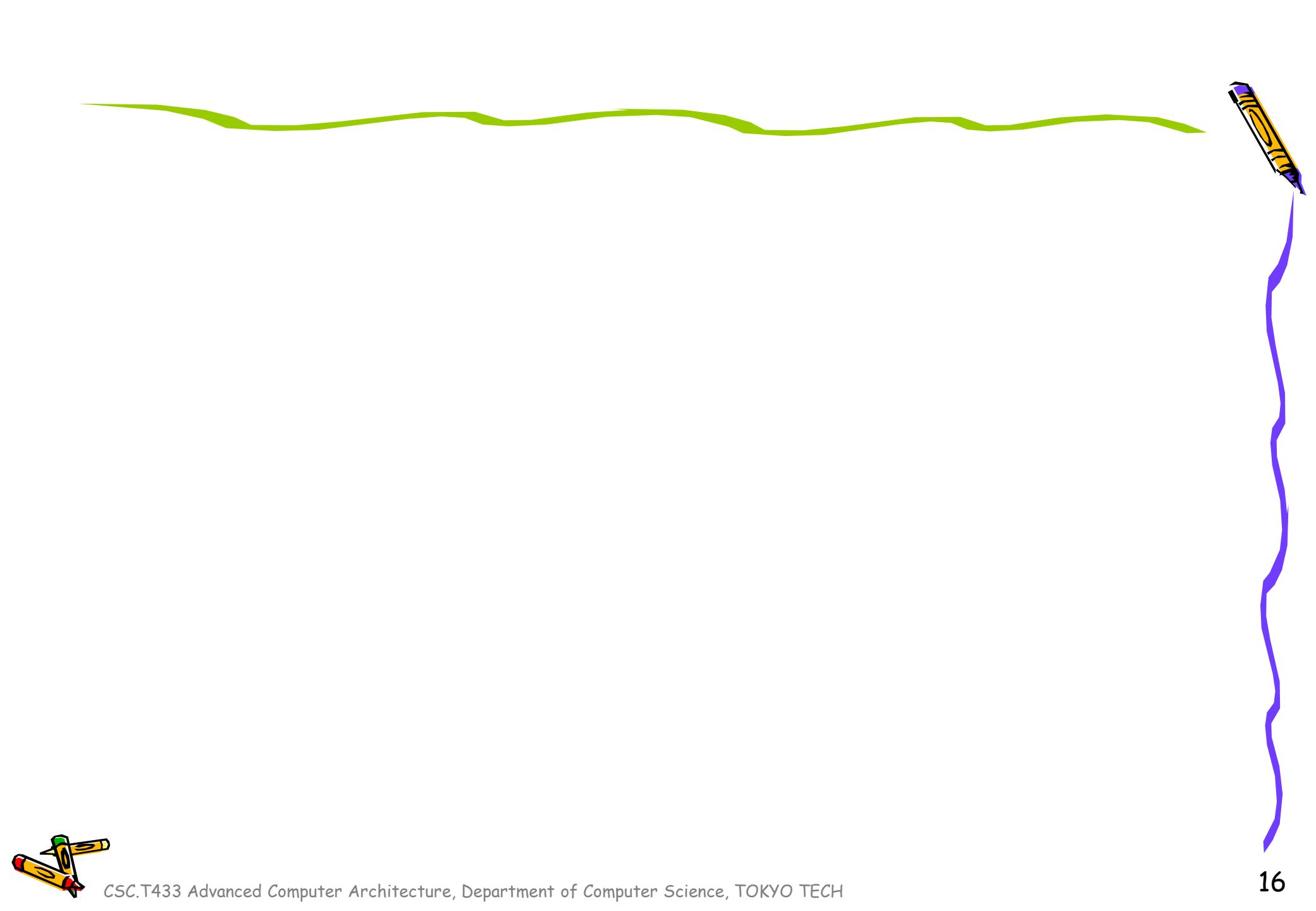

The key : pipeline registers

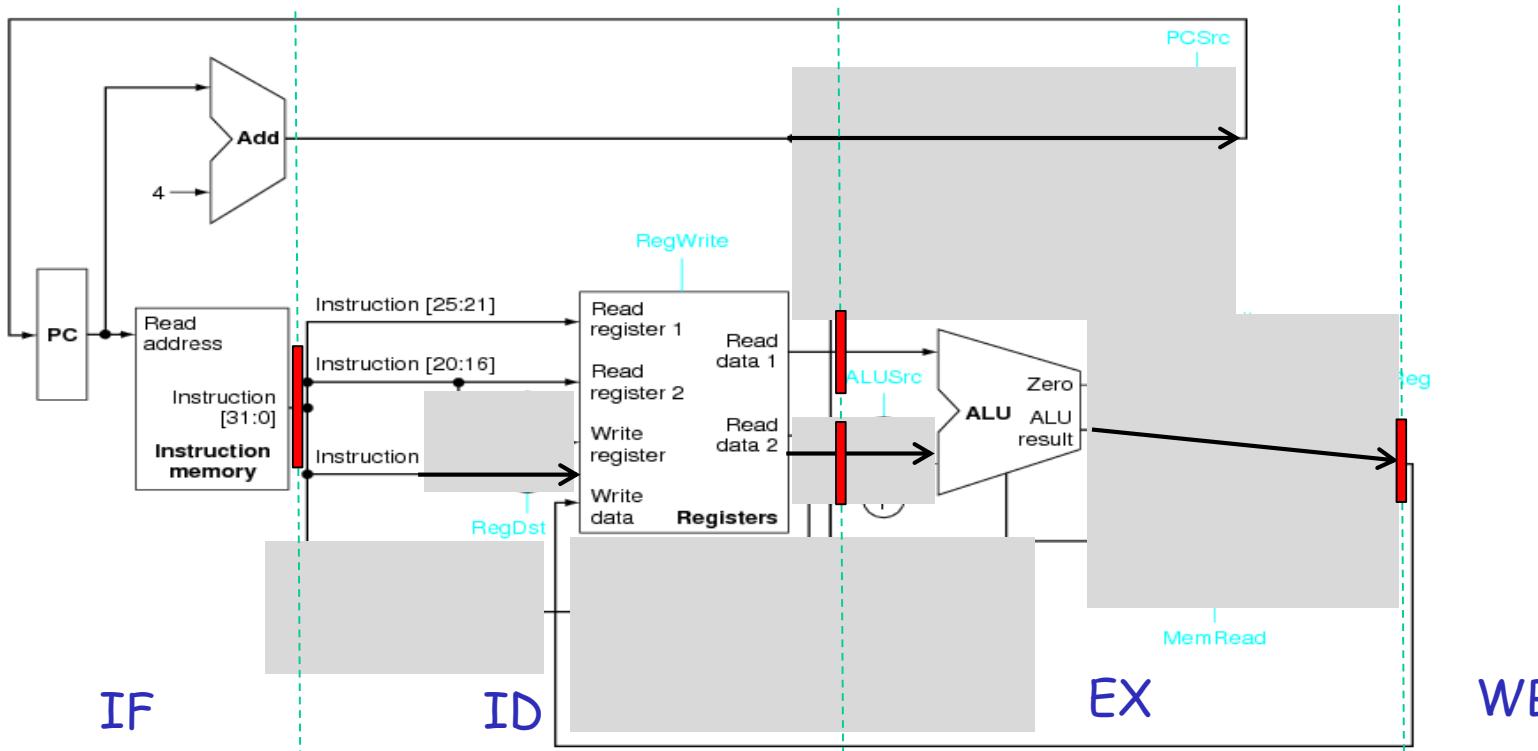


Execution behavior of a pipelining processor

- [1] 0x00: add \$0, \$0, \$0 # NOP, \$0 <= 0 + 0
- [2] 0x04: add \$1, \$1, \$1 # \$1 <= 22 + 22
- [3] 0x08: add \$2, \$2, \$2 # \$2 <= 33 + 33
- [4] 0x0c: add \$0, \$0, \$0 # NOP
- [5] 0x10: add \$0, \$0, \$0 # NOP
- [6] 0x14: add \$0, \$0, \$0 # NOP

assuming that the initial values of $r[1]=22$ and $r[2]=33$

cc1

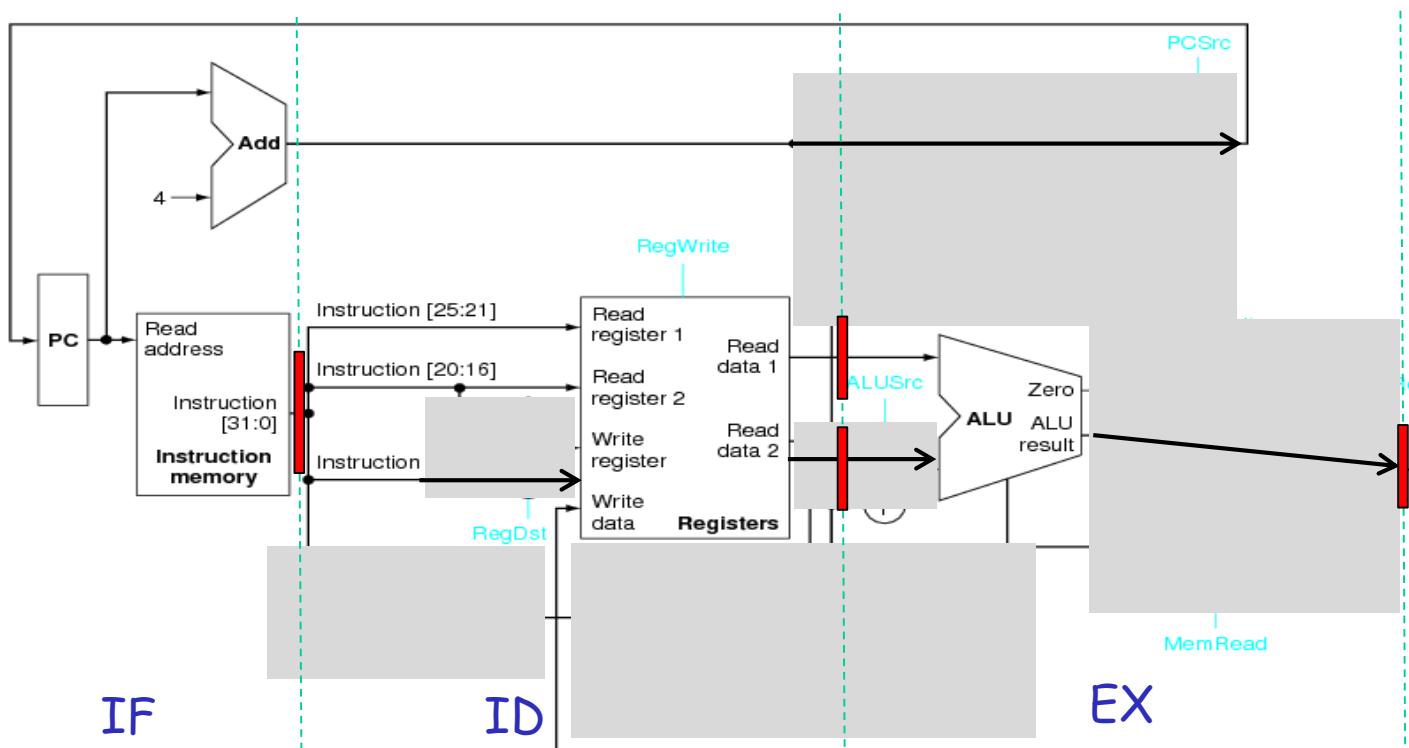


Execution behavior of a pipelining processor

- [1] 0x00: add \$0, \$0, \$0 # NOP, \$0 <= 0 + 0
- [2] 0x04: add \$1, \$1, \$1 # \$1 <= 22 + 22
- [3] 0x08: add \$2, \$2, \$2 # \$2 <= 33 + 33
- [4] 0x0c: add \$0, \$0, \$0 # NOP
- [5] 0x10: add \$0, \$0, \$0 # NOP
- [6] 0x14: add \$0, \$0, \$0 # NOP

assuming that the initial values of $r[1]=22$ and $r[2]=33$

cc1

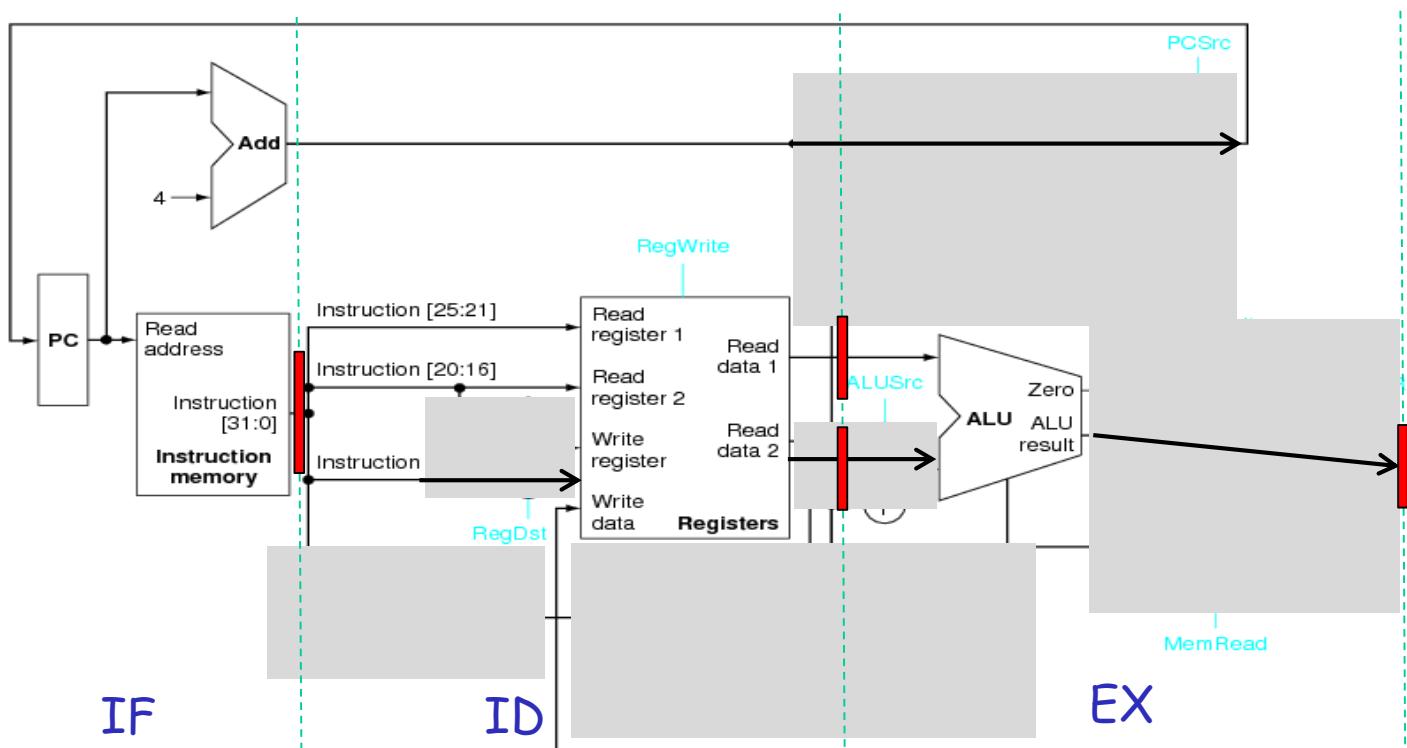


Execution behavior of a pipelining processor

- [1] 0x00: add \$0, \$0, \$0 # NOP, \$0 <= 0 + 0
- [2] 0x04: add \$1, \$1, \$1 # \$1 <= 22 + 22
- [3] 0x08: add \$2, \$2, \$2 # \$2 <= 33 + 33
- [4] 0x0c: add \$0, \$0, \$0 # NOP
- [5] 0x10: add \$0, \$0, \$0 # NOP
- [6] 0x14: add \$0, \$0, \$0 # NOP

assuming that the initial values of $r[1]=22$ and $r[2]=33$

cc2

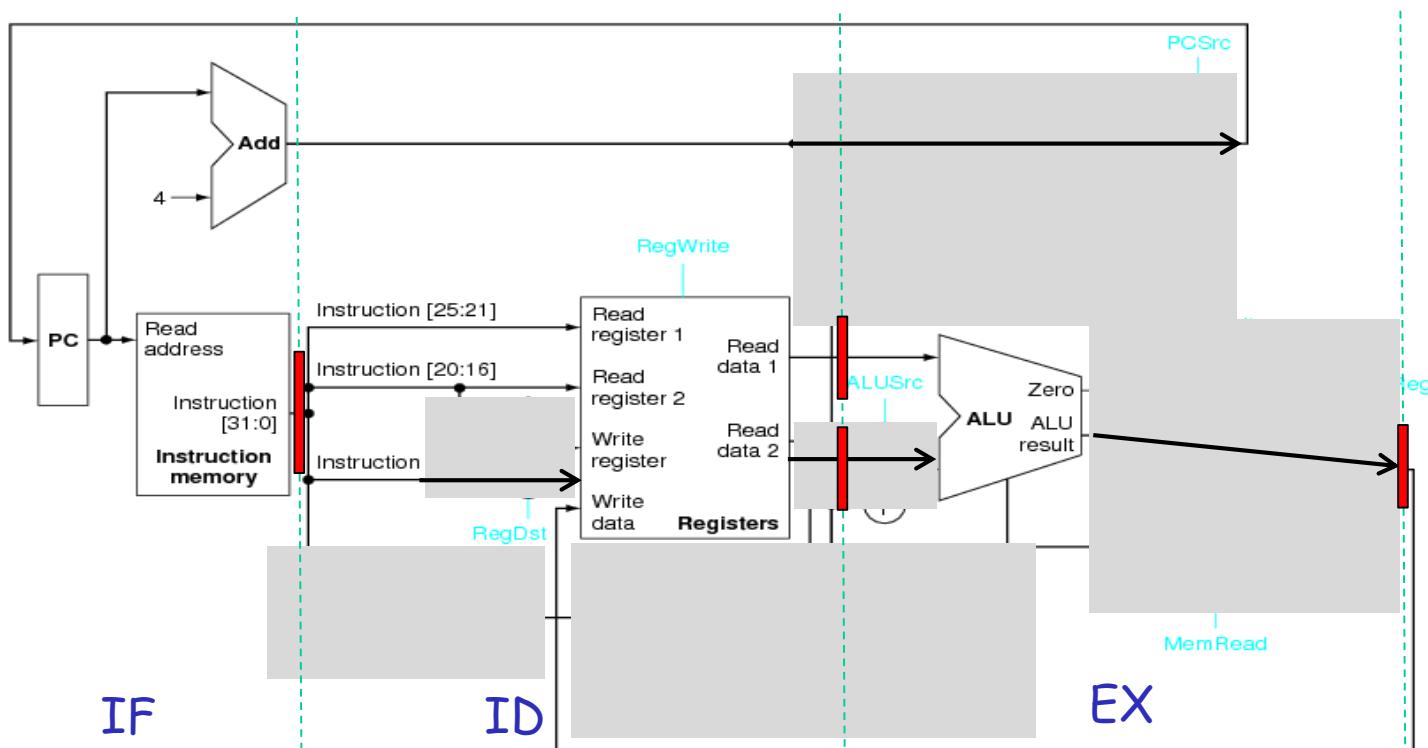


Execution behavior of a pipelining processor

- [1] 0x00: add \$0, \$0, \$0 # NOP, \$0 <= 0 + 0
- [2] 0x04: add \$1, \$1, \$1 # \$1 <= 22 + 22
- [3] 0x08: add \$2, \$2, \$2 # \$2 <= 33 + 33
- [4] 0x0c: add \$0, \$0, \$0 # NOP
- [5] 0x10: add \$0, \$0, \$0 # NOP
- [6] 0x14: add \$0, \$0, \$0 # NOP

assuming that the initial values of $r[1]=22$ and $r[2]=33$

cc3

 


Execution behavior of a pipelining processor

- [1] 0x00: add \$0, \$0, \$0 # NOP, \$0 <= 0 + 0
- [2] 0x04: add \$1, \$1, \$1 # \$1 <= 22 + 22
- [3] 0x08: add \$2, \$2, \$2 # \$2 <= 33 + 33
- [4] 0x0c: add \$0, \$0, \$0 # NOP
- [5] 0x10: add \$0, \$0, \$0 # NOP
- [6] 0x14: add \$0, \$0, \$0 # NOP

assuming that the initial values of $r[1]=22$ and $r[2]=33$

cc4

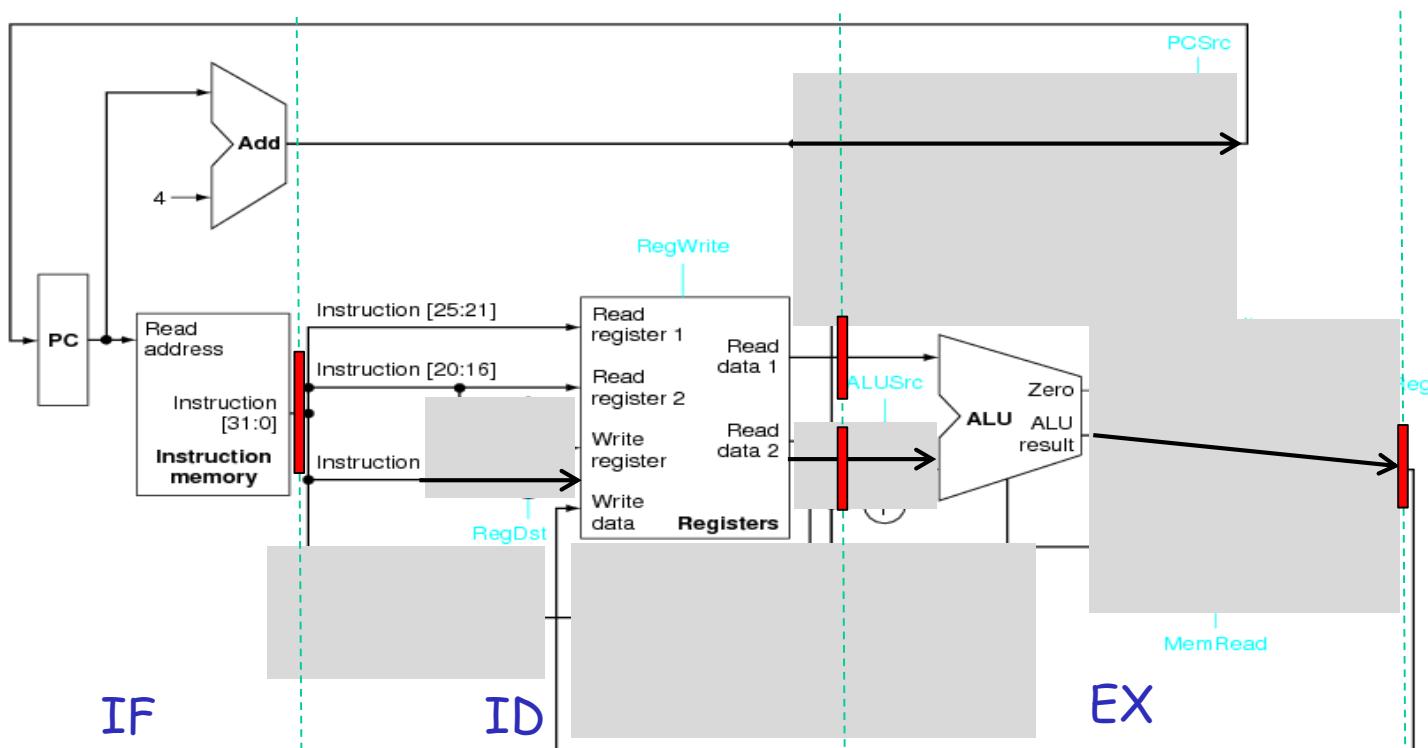



Execution behavior of a pipelining processor

- [1] 0x00: add \$0, \$0, \$0 # NOP, \$0 <= 0 + 0
- [2] 0x04: add \$1, \$1, \$1 # \$1 <= 22 + 22
- [3] 0x08: add \$2, \$2, \$2 # \$2 <= 33 + 33
- [4] 0x0c: add \$0, \$0, \$0 # NOP
- [5] 0x10: add \$0, \$0, \$0 # NOP
- [6] 0x14: add \$0, \$0, \$0 # NOP


assuming that the initial values of $r[1]=22$ and $r[2]=33$


cc5

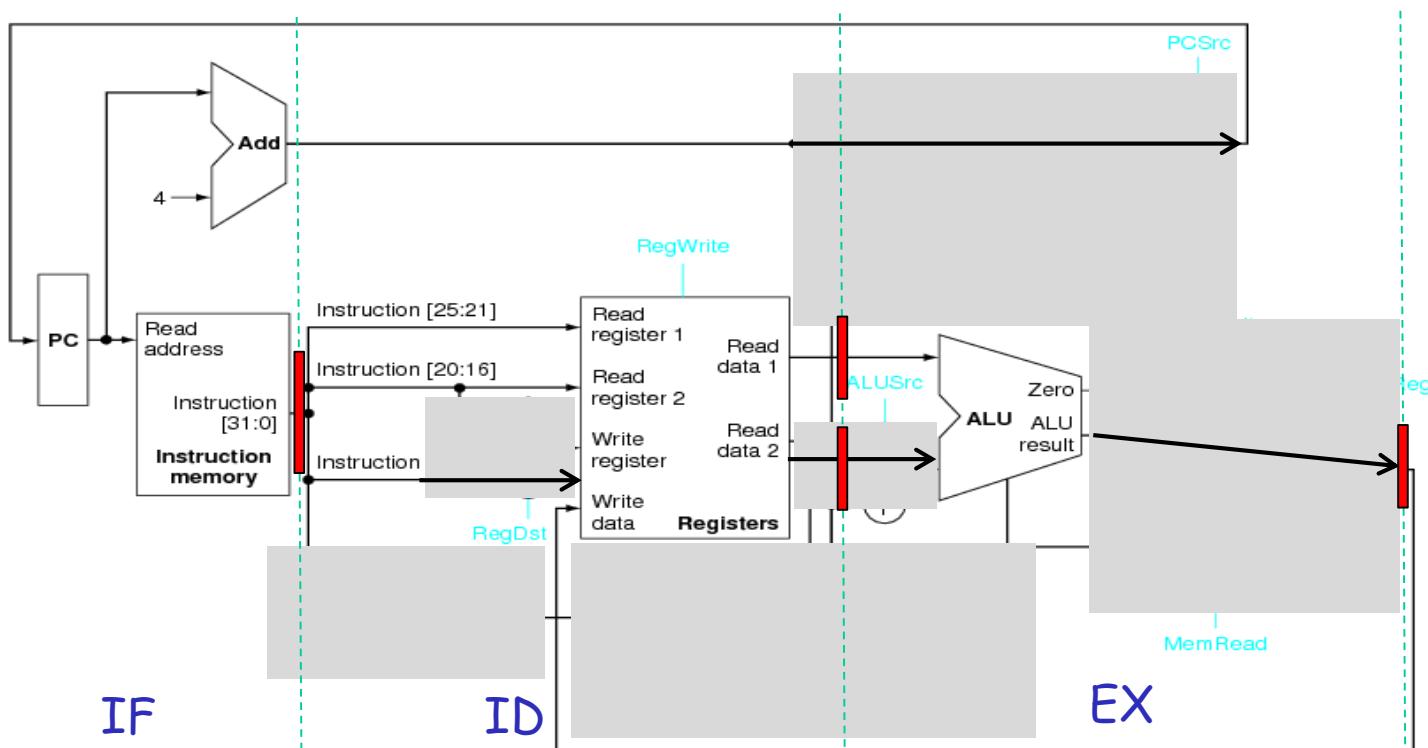

 

Single-cycle and pipelined processors

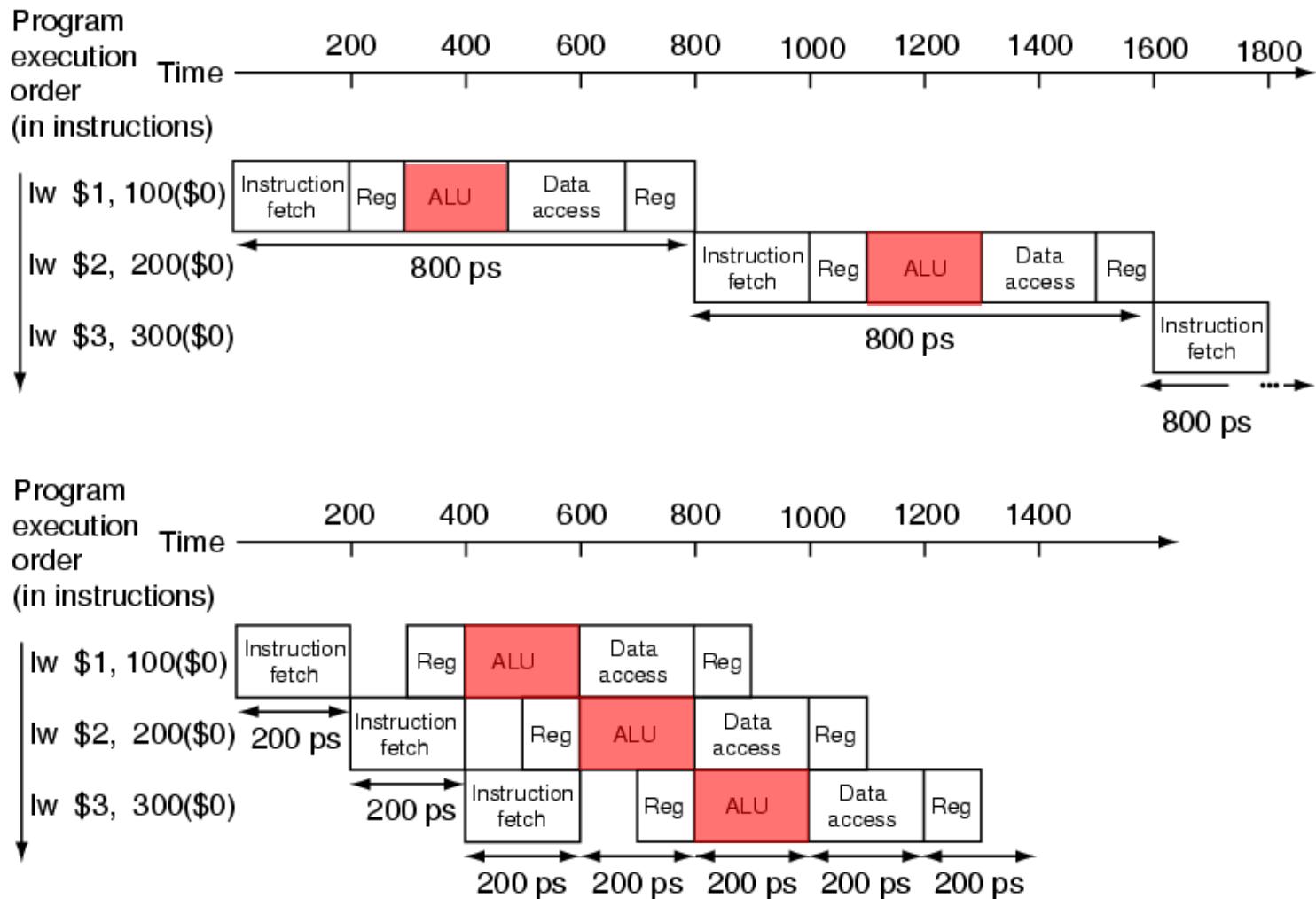

 

Assignment 3

1. Design a four stage pipelined processor supporting MIPS `add` instructions in Verilog HDL. Please download `proc01.v` from the support page and refer it.
2. Verify the behavior of designed processor using following assembly code
assuming initial values of $r[1]=22$, $r[2]=33$, $r[3]=44$, and $r[4]=55$
 - `add $0, $0, $0 # NOP {6'h0, 5'd0, 5'd0, 5'd0, 5'd0, 6'h20}`
 - `add $1, $1, $1 #`
 - `add $2, $2, $2 #`
 - `add $3, $3, $3 #`
 - `add $4, $4, $4 #`
3. Submit **your report** in a PDF file via E-mail by the next Monday.
 - The report should include a block diagram, a source code in Verilog HDL, and obtained waveforms of your design.
 - E-mail address : `report@arch.cs.titech.ac.jp`
 - E-mail title: Assignment of Advanced Computer Architecture



