

2024年度(令和6年)版

Ver. 2024-10-25b

Course number: CSC.T363

コンピュータアーキテクチャ Computer Architecture

7. パイプラインプロセッサ Pipelined Processor

www.arch.cs.titech.ac.jp/lecture/CA/
Tue 13:30-15:10, 15:25-17:05
Fri 13:30-15:10

吉瀬 謙二 情報工学系
Kenji Kise, Department of Computer Science
kise_at_c.titech.ac.jp

RISC-V の命令長



The RISC-V Instruction Set Manual
Volume I: Unprivileged ISA
Document Version 20191214-draft

Editors: Andrew Waterman¹, Krste Asanović^{1,2}

¹SiFive Inc.,

²CS Division, EECS Department, University of California, Berkeley

andrew@sifive.com, krste@berkeley.edu

November 12, 2021

 


Figure 1.1: RISC-V instruction length encoding. Only the 16-bit and 32-bit encodings are considered frozen at this time.



A Typical Memory Hierarchy

- By taking advantage of **the principle of locality** (局所性)
 - Present **much memory** in **the cheapest technology**
 - at **the speed of fastest technology**



Speed (%cycles): $\frac{1}{2}$'s

1's

10's

100's

1,000's

Size (bytes): 100's

K's

10K's

M's

G's to T's


Cost: highest

lowest

TLB: Translation Lookaside Buffer

proc5s: single-cycle processor

 
- supporting **add, addi, lw, sw, bne** instructions



```
module m_proc5s(w_clk);
    input wire w_clk;
    wire [31:0] w_npc, w_ir, w_imm, w_r1, w_r2, w_s2, w_rt;
    wire [31:0] w_alu, w_ldd, w_tpc, w_pcin;
    wire w_tkn;
    reg [31:0] r_pc=0; // m1
    assign w_pcin = (w_b & w_tkn) ? w_tpc : w_npc; // m11
    assign w_npc = r_pc + 32'h4; // m2
    m_am_imem m3 (r_pc, w_ir);
    wire w_r, w_i, w_s, w_b, w_u, w_j, w_ld;
    m_gen_imm m4 (w_ir, w_imm, w_r, w_i,
                  w_s, w_b, w_u, w_j, w_ld);
    m_RF m5 (w_clk, w_ir[19:15], w_ir[24:20], w_r1, w_r2,
             w_ir[11:7], !w_s & !w_b, w_rt);
    assign w_tpc = r_pc + w_imm; // m6
    assign w_s2 = (!w_r & !w_b) ? w_imm : w_r2; // m7
    m_alu m8 (w_r1, w_s2, w_alu, w_tkn);
    m_am_dmem m9 (w_clk, w_alu, w_s, w_r2, w_ldd);
    assign w_rt = (w_ld) ? w_ldd : w_alu; // m10
    always @(posedge w_clk) r_pc <= w_pcin;
endmodule
```

Clock rate is mainly determined by

 - Switching speed of gates (transistors)
- **The number of levels of gates**
 - The maximum number of gates cascaded in series in any combinational logics.
 - In this example, the number of levels of gates is 3.
- Wiring delay and fanout




プロセッサが命令を処理するための5つのステップ

- **IF (Instruction Fetch)**
メモリから命令をフェッチする.
- **ID (Instruction Decode)**
命令をデコード(解読)しながら, レジスタの値を読み出す.
- **EX (Execution)**
命令操作の実行またはアドレスの生成を行う.
- **MA (Memory Access)**
必要であれば, データ・メモリ中のオペランドにアクセスする.
- **WB (Write Back)**
必要であれば, 結果をレジスタに書き込む.





proc8: 4-stage pipelining processor

 

Source code is available here.



<https://gihyo.jp/book/2024/978-4-297-14008-3/support>

proc8: 4-stage pipelining processor

  


data forwarding

proc8: 4-stage pipelining processor

  


RF2 (Register File) with bypassing

 

```
module m_RF2(w_clk, w_radr1, w_radr2, w_rd1, w_rd2, w_wadr, w_we, w_wd);
  input  wire w_clk, w_we;
  input  wire [4:0] w_radr1, w_radr2, w_wadr;
  output wire [31:0] w_rd1, w_rd2;
  input  wire [31:0] w_wd;
  reg [31:0] mem [0:31];
  wire w_bp1 = (w_we & w_radr1==w_wadr);
  wire w_bp2 = (w_we & w_radr2==w_wadr);
  assign w_rd1 = (w_radr1==5'd0) ? 32'd0 : (w_bp1) ? w_wd : mem[w_radr1];
  assign w_rd2 = (w_radr2==5'd0) ? 32'd0 : (w_bp2) ? w_wd : mem[w_radr2];
  always @(posedge w_clk) if (w_we) mem[w_wadr] <= w_wd;
  always @(posedge w_clk) if (w_we & w_wadr==5'd30) $finish;
  integer i; initial for (i=0; i<32; i=i+1) mem[i] = 32'd0;
endmodule
```



 


```

module m_proc8s(w_clk);
    input wire w_clk;
    reg [31:0] P1_ir=32'h13, P1_pc=0, P2_pc=0, P3_pc=0;
    reg [31:0] P2_r1=0, P2_s2=0, P2_r2=0, P2_tpc=0;
    reg [31:0] P3_alu=0, P3_ldd=0;
    reg P2_r=0, P2_s=0, P2_b=0, P2_ld=0, P3_s=0, P3_b=0, P3_ld=0;
    reg [4:0] P2_rd=0, P2_rs1=0, P2_rs2=0, P3_rd=0;
    reg P1_v=0, P2_v=0, P3_v=0;
    wire [31:0] w_npc, w_ir, w_imm, w_r1, w_r2, w_s2, w_rt;
    wire [31:0] w_alu, w_ldd, w_tpc, w_pcin, w_in1, w_in2, w_in3;
    wire w_r, w_i, w_s, w_b, w_u, w_j, w_ld, w_tkn;
    reg [31:0] r_pc = 0; // m1
    wire w_miss = P2_b & w_tkn & P2_v;
    assign w_pcin = (w_miss) ? P2_tpc : w_npc; // m0
    assign w_npc = r_pc + 32'h4; // m2
    m_am_imem m3 (r_pc, w_ir);
    m_gen_imm m4 (P1_ir, w_imm, w_r, w_i, w_s, w_b, w_u, w_j, w_ld);
    m_RF2 m5 (w_clk, P1_ir[19:15], P1_ir[24:20], w_r1, w_r2,
              P3_rd, !P3_s & !P3_b & P3_v, w_rt);
    assign w_tpc = P1_pc + w_imm; // m6
    assign w_s2 = (!w_r & !w_b) ? w_imm : w_r2; // m7
    always @(posedge w_clk) begin
        {P1_v, P2_v, P3_v} <= {!w_miss, !w_miss & P1_v, P2_v};
        {r_pc, P1_ir, P1_pc, P2_pc} <= {w_pcin, w_ir, r_pc, P1_pc};
        {P2_r1, P2_r2, P2_s2, P2_tpc} <= {w_r1, w_r2, w_s2, w_tpc};
        {P2_r, P2_s, P2_b, P2_ld} <= {w_r, w_s, w_b, w_ld};
        {P2_rs2, P2_rs1, P2_rd} <= {P1_ir[24:15], P1_ir[11:7]};
        {P3_pc, P3_ld} <= {P2_pc, P2_ld};
        {P3_alu, P3_ldd, P3_rd} <= {w_alu, w_ldd, P2_rd};
    end
    assign w_alu = w_in1 + w_in2; // m8
    assign w_tkn = w_in1 != w_in2; // m8
    m_am_dmem m9 (w_clk, w_alu, P2_s & P2_v, w_in3, w_ldd);
    assign w_rt = (P3_ld) ? P3_ldd : P3_alu; // m10
    assign w_in1 = (!P3_rd & P2_rs1==P3_rd) ? w_rt : P2_r1; // m11
    assign w_in3 = (!P3_rd & P2_rs2==P3_rd) ? w_rt : P2_r2; // m13
    assign w_in2 = (!P3_rd & (P2_r|P2_b) & P2_rs2==P3_rd) ? w_rt : P2_s2; // m12
endmodule

```



 

```

module m_proc8s(w_clk);
    input wire w_clk;
    reg [31:0] P1_ir=32'h13, P1_pc=0, P2_pc=0, P3_pc=0;
    reg [31:0] P2_r1=0, P2_s2=0, P2_r2=0, P2_tpc=0;
    reg [31:0] P3_alu=0, P3_ldd=0;
    reg P2_r=0, P2_s=0, P2_b=0, P2_ld=0, P3_s=0, P3_b=0, P3_ld=0;
    reg [4:0] P2_rd=0, P2_rs1=0, P2_rs2=0, P3_rd=0;
    reg P1_v=0, P2_v=0, P3_v=0;
    wire [31:0] w_npc, w_ir, w_imm, w_r1, w_r2, w_s2, w_rt;
    wire [31:0] w_alu, w_ldd, w_tpc, w_pcin, w_in1, w_in2, w_in3;
    wire w_r, w_i, w_s, w_b, w_u, w_j, w_ld, w_tkn;
    reg [31:0] r_pc = 0; // m1
    wire w_miss = P2_b & w_tkn & P2_v;
    assign w_pcin = (w_miss) ? P2_tpc : w_npc; // m0
    assign w_npc = r_pc + 32'h4; // m2
    m_am_imem m3 (r_pc, w_ir);
    m_gen_imm m4 (P1_ir, w_imm, w_r, w_i, w_s, w_b, w_u, w_j, w_ld);
    m_RF2 m5 (w_clk, P1_ir[19:15], P1_ir[24:20], w_r1, w_r2,
              P3_rd, !P3_s & !P3_b & P3_v, w_rt);
    assign w_tpc = P1_pc + w_imm; // m6
    assign w_s2 = (!w_r & !w_b) ? w_imm : w_r2; // m7
    always @(posedge w_clk) begin
        {P1_v, P2_v, P3_v} <= {!w_miss, !w_miss & P1_v, P2_v};
        {r_pc, P1_ir, P1_pc, P2_pc} <= {w_pcin, w_ir, r_pc, P1_pc};
        {P2_r1, P2_r2, P2_s2, P2_tpc} <= {w_r1, w_r2, w_s2, w_tpc};
        {P2_r, P2_s, P2_b, P2_ld} <= {w_r, w_s, w_b, w_ld};
        {P2_rs2, P2_rs1, P2_rd} <= {P1_ir[24:15], P1_ir[11:7]};
        {P3_pc, P3_ld} <= {P2_pc, P2_ld};
        {P3_alu, P3_ldd, P3_rd} <= {w_alu, w_ldd, P2_rd};
    end
    assign w_alu = w_in1 + w_in2; // m8
    assign w_tkn = w_in1 != w_in2; // m8
    m_am_dmem m9 (w_clk, w_alu, P2_s & P2_v, w_in3, w_ldd);
    assign w_rt = (P3_ld) ? P3_ldd : P3_alu; // m10
    assign w_in1 = (!P3_rd & P2_rs1==P3_rd) ? w_rt : P2_r1; // m11
    assign w_in3 = (!P3_rd & P2_rs2==P3_rd) ? w_rt : P2_r2; // m13
    assign w_in2 = (!P3_rd & (P2_r|P2_b) & P2_rs2==P3_rd) ? w_rt : P2_s2; // m12
endmodule

```



 

```

module m_proc8s(w_clk);
    input wire w_clk;
    reg [31:0] P1_ir=32'h13, P1_pc=0, P2_pc=0, P3_pc=0;
    reg [31:0] P2_r1=0, P2_s2=0, P2_r2=0, P2_tpc=0;
    reg [31:0] P3_alu=0, P3_ldd=0;
    reg P2_r=0, P2_s=0, P2_b=0, P2_ld=0, P3_s=0, P3_b=0, P3_ld=0;
    reg [4:0] P2_rd=0, P2_rs1=0, P2_rs2=0, P3_rd=0;
    reg P1_v=0, P2_v=0, P3_v=0;
    wire [31:0] w_npc, w_ir, w_imm, w_r1, w_r2, w_s2, w_rt;
    wire [31:0] w_alu, w_ldd, w_tpc, w_pcin, w_in1, w_in2, w_in3;
    wire w_r, w_i, w_s, w_b, w_u, w_j, w_ld, w_tkn;
    reg [31:0] r_pc = 0; // m1
    wire w_miss = P2_b & w_tkn & P2_v;
    assign w_pcin = (w_miss) ? P2_tpc : w_npc; // m0
    assign w_npc = r_pc + 32'h4; // m2
    m_am_imem m3 (r_pc, w_ir);
    m_gen_imm m4 (P1_ir, w_imm, w_r, w_i, w_s, w_b, w_u, w_j, w_ld);
    m_RF2 m5 (w_clk, P1_ir[19:15], P1_ir[24:20], w_r1, w_r2,
              P3_rd, !P3_s & !P3_b & P3_v, w_rt);
    assign w_tpc = P1_pc + w_imm; // m6
    assign w_s2 = (!w_r & !w_b) ? w_imm : w_r2; // m7
    always @(posedge w_clk) begin
        {P1_v, P2_v, P3_v} <= {!w_miss, !w_miss & P1_v, P2_v};
        {r_pc, P1_ir, P1_pc, P2_pc} <= {w_pcin, w_ir, r_pc, P1_pc};
        {P2_r1, P2_r2, P2_s2, P2_tpc} <= {w_r1, w_r2, w_s2, w_tpc};
        {P2_r, P2_s, P2_b, P2_ld} <= {w_r, w_s, w_b, w_ld};
        {P2_rs2, P2_rs1, P2_rd} <= {P1_ir[24:15], P1_ir[11:7]};
        {P3_pc, P3_ld} <= {P2_pc, P2_ld};
        {P3_alu, P3_ldd, P3_rd} <= {w_alu, w_ldd, P2_rd};
    end
    assign w_alu = w_in1 + w_in2; // m8
    assign w_tkn = w_in1 != w_in2; // m8
    m_am_dmem m9 (w_clk, w_alu, P2_s & P2_v, w_in3, w_ldd);
    assign w_rt = (P3_ld) ? P3_ldd : P3_alu; // m10
    assign w_in1 = (!P3_rd & P2_rs1==P3_rd) ? w_rt : P2_r1; // m11
    assign w_in3 = (!P3_rd & P2_rs2==P3_rd) ? w_rt : P2_r2; // m13
    assign w_in2 = (!P3_rd & (P2_r|P2_b) & P2_rs2==P3_rd) ? w_rt : P2_s2; // m12
endmodule

```



proc8: 4-stage pipelining processor




Processor simulation

```
// 00  addi x1,x0,3
// 04  add  x2,x1,x1
// 08  addi x10,x2,5
// 0c  HALT
```

```
$ iverilog -DP1 proc8s.v
$ ./a.out
```


CC01	00000000	00000000	00000000	00000000	0	0	0
CC02	00000004	00000000	00000000	00000000	0	0	0
CC03	00000008	00000004	00000000	00000000	0	3	3
CC04	0000000c	00000008	00000004	00000000	3	3	6
CC05	00000010	0000000c	00000008	00000004	6	5	11
CC06	00000014	00000010	0000000c	00000008	11	0	11
CC07	00000018	00000014	00000010	0000000c	0	0	0

 

```
module m_sim(w_clk, w_cc); /* please wrap me by m_top_wrapper */
    input wire w_clk; input wire [31:0] w_cc;
    m_proc8s m (w_clk);
    initial begin
        `define MM m.m3.mem
        `include "asm.txt"
    end
    initial #99 forever #100 $display("CC%02d %h %h %h %h %d %d %d",
        w_cc, m.r_pc, m.P1_pc, m.P2_pc, m.P3_pc,
        m.w_in1, m.w_in2, m.w_alu);
endmodule
```

module **m_rvcore** (RV32I, single-cycle processor)

- **50MHz** operating frequency

 

RVCore_Base, RISC-V RV32I Baseline

```

/*****
 * RVCore_Base, RISC-V RV32I Baseline Version v2024-10-22a      ArchLab, Science Tokyo */
/*****

`default_nettype none

`define VERIFY           // define this to generate verify.txt
`define MEM_TXT          "sample1.txt" // file name of memory initialization file
`define MEM_SIZE         4096         // 4KB instruction memory and 4KB data memory
`define START_PC         0            // initial PC value
`define UART_CNT         50           // UART wait count, 50MHz / 500 = 1Mbaud
`define D_I_TYPE         0
`define D_R_TYPE         1
`define D_S_TYPE         2
`define D_B_TYPE         3
`define D_J_TYPE         4
`define D_U_TYPE         5
`define D_JA_IS          6
`define D_LD_IS          7
`define D_MUL_IS         8
`define D_DIV_IS         9

```

```

/*****
`ifdef VERIFY
  initial $write("\n== VERIFY is defined and generate verify.txt\n");
  integer fd;
  initial fd = $fopen("verify.txt", "w");
  reg [31:0] r_tc = 1;
  always @(posedge w_clk) if(!r_rst) r_tc <= r_tc + 1;
  integer i, j;
  always @(posedge w_clk) if(!r_rst) begin
    $fwrite(fd, "%08d %08x %08x\n", r_tc, r_pc, w_ir);
    for (i=0; i<4; i=i+1) for (j=0; j<8; j=j+1) begin
      $fwrite(fd, "%08x", ((i*8+j) == [27'd0, w_rd]) && (i*8+j != 0)) ?
        w_ma_rslt : regfile1.mem[i * 8 + j]);
      $fwrite(fd, "%s", (j != 7 ? " " : "\n"));
    end
  end
`endif
endmodule

```

proc.v

```

module m_rvcore ( //RVCore Simple Version
  input wire w_clk, w_rst,
  input wire [31:0] I_IN, D_IN,
  output wire [31:0] I_ADDR, D_ADDR,
  output wire [31:0] D_OUT,
  output wire [3:0] D_WE);

  reg r_rst = 1;
  always @(posedge w_clk) r_rst <= w_rst;

  reg [31:0] r_pc = `START_PC;
  always @(posedge w_clk) r_pc <= (r_rst) ? `START_PC : (w_b_rslt) ? w_tkn_pc : r_pc+4;
  assign I_ADDR = r_pc;

  wire [31:0] w_ir = I_IN;
  wire [31:0] w_rrs1, w_rrs2_t, w_imm_t, w_rslt;
  wire [4:0] w_rs1, w_rs2, w_rd;
  wire w_op_im;
  wire [9:0] w_i_type;
  wire [10:0] w_alu_c;
  wire [6:0] w_bruc;
  wire w_b_rslt;
  wire w_ia = w_i_type[6];
  wire [4:0] w_op = w_ir[6:2];
  wire [31:0] w_imm = (w_ia) ? r_pc+4 : (w_op==5'b00101) ? r_pc+w_imm_t : w_imm_t;
  wire [31:0] w_rrs2 = (w_op_im) ? w_imm : w_rrs2_t;

  m_decode decode1 (w_ir, w_rd, w_rs1, w_rs2, w_op_im, w_i_type, w_alu_c, w_bruc, w_imm_t);

  m_regfile regfile (w_clk, w_rs1, w_rs2, w_rrs1, w_rrs2_t, w_ma_rd, w_ma_rslt);

  m_alu alu1 (w_rrs1, w_rrs2, w_alu_c, w_rslt);

  /**** for branch and jump instructions ****/
  wire [31:0] w_tkn_pc = (w_ir[6:2]==5'b11001) ? w_rrs1+w_imm_t : r_pc+w_imm_t;
  m_bru bru0(w_rrs1, w_rrs2, w_bruc, w_b_rslt);

  /**** for load and store instructions ****/
  wire [2:0] w_fct3 = w_ir[14:12];
  wire [31:0] w_mem_addr = w_rrs1 + w_imm;
  wire w_we0 = (w_i_type[`D_S_TYPE] & w_fct3[1:0]==0);
  wire w_we1 = (w_i_type[`D_S_TYPE] & w_fct3[0]);
  wire w_we2 = (w_i_type[`D_S_TYPE] & w_fct3[1]);
  wire [3:0] w_we_sb = (w_we0) ? 4'b0001 << D_ADDR[1:0] : 0;
  wire [3:0] w_we_sh = (w_we1) ? 4'b0011 << [D_ADDR[1], 1'b0] : 0;
  wire [3:0] w_we_sw = (w_we2) ? 4'b1111 : 0;

  assign D_WE = (w_we_sh ^ w_we_sw ^ w_we_sb);
  assign D_ADDR = w_mem_addr;
  assign D_OUT = (w_fct3[0]) ? {2[w_rrs2[15:0]] : (w_fct3[1]) ? w_rrs2 : {4[w_rrs2[7:0]]}};

  /**** for load instructions ****/
  wire [15:0] w_ma_lh_t = (w_mem_addr[1]) ? D_IN[31:16] : D_IN[15:0]; // align
  wire [7:0] w_ma_lb_t = (w_mem_addr[0]) ? w_ma_lh_t[15:8] : w_ma_lh_t[7:0]; // align
  wire [31:0] w_ma_lb = (w_fct3==3'b000) ? {[24{w_ma_lb_t[7:0]}] : 0;
  wire [31:0] w_ma_lbu = (w_fct3==3'b100) ? {24'd0, w_ma_lb_t[7:0]} : 0;
  wire [31:0] w_ma_lh = (w_fct3==3'b001) ? {[16{w_ma_lh_t[15]}] : 0;
  wire [31:0] w_ma_lhu = (w_fct3==3'b101) ? {16'd0, w_ma_lh_t[15:0]} : 0;
  wire [31:0] w_ma_lw = (w_fct3==3'b010) ? D_IN : 0;
  wire [31:0] w_ma_ld_rslt = w_ma_lb ^ w_ma_lbu ^ w_ma_lh ^ w_ma_lhu ^ w_ma_lw;

  wire [31:0] w_ma_rslt_t = (w_i_type[`D_LD_IS]) ? w_ma_ld_rslt : w_rslt;

  wire [4:0] w_ma_rd = w_rd;
  wire [31:0] w_ma_rslt = (w_rd!=0) ? w_ma_rslt_t : 0;

```

RVCore_Base, RISC-V RV32I Baseline Version v2024-10-22a

```

/*****
`ifdef VERIFY
initial $write("%n= VERIFY is defined and generate verify.txt\n");
integer fd;
initial fd = $fopen("verify.txt", "w");
reg [31:0] r_tc = 1;
always @(posedge w_clk) if(!r_rst) r_tc <= r_tc + 1;
integer i, j;
always @(posedge w_clk) if(!r_rst) begin
    $fwrite(fd, "%08d %08x %08x\n", r_tc, r_pc, w_ir);
    for (i=0; i<4; i=i+1) for (j=0; j<8; j=j+1) begin
        $fwrite(fd, "%08x", ((i*8+j == {27'd0, w_rd}) && (i*8+j != 0)) ?
            w_ma_rslt : regfile1.mem[i * 8 + j]);
        $fwrite(fd, "%s", (j != 7 ? " " : "\n"));
    end
end
`endif
endmodule

```

proc.v

verify.txt

```

00000090 000000dc 00150513
00000000 00000968 00000f20 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000bc7 00000000 00000000 40008000 00010000 00000075
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000091 000000e0 fe0798e3
00000000 00000968 00000f20 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000bc7 00000000 00000000 40008000 00010000 00000075
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000092 000000d0 00e7e7b3
00000000 00000968 00000f20 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000bc7 00000000 00000000 40008000 00010000 00010075
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000093 000000d4 00f6a023
00000000 00000968 00000f20 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000bc7 00000000 00000000 40008000 00010000 00010075
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000094 000000d8 00154783
00000000 00000968 00000f20 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000bc7 00000000 00000000 40008000 00010000 00000065
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000095 000000dc 00150513
00000000 00000968 00000f20 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000bc8 00000000 00000000 40008000 00010000 00000065
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000000 00000000 00000000 00000000 00000000 00000000 00000000 00000000
00000096 000000e0 fe0798e3
00000000 00000968 00000f20 00000000 00000000 00000000 00000000 00000000

```

RVCore_Base, RISC-V RV32I Baseline Version v2024-10-22a



```
module m_imem (
    input wire w_clk,
    input wire w_we,
    input wire [9:0] w_adr,
    input wire [31:0] w_din,
    output wire [31:0] w_dout
);
    reg [31:0] mem [0:1023];
    `ifndef SYNTHESIS
    initial begin
        `include `MEM_TXT
    end
    `endif

    always @(posedge w_clk) if (w_we) mem[w_adr] <= w_din;
    assign w_dout = mem[w_adr];
endmodule

module m_dmem (
    input wire w_clk,
    input wire [3:0] w_we,
    input wire [9:0] w_adr,
    input wire [31:0] w_din,
    output wire [31:0] w_dout
);
    reg [31:0] mem [0:1023];
    `ifndef SYNTHESIS
    initial begin
        `include `MEM_TXT
    end
    `endif

    always @(posedge w_clk) begin
        if (w_we[0]) mem[w_adr][7:0] <= w_din[7:0];
        if (w_we[1]) mem[w_adr][15:8] <= w_din[15:8];
        if (w_we[2]) mem[w_adr][23:16] <= w_din[23:16];
        if (w_we[3]) mem[w_adr][31:24] <= w_din[31:24];
    end
    assign w_dout = mem[w_adr];
endmodule
```

proc.v

sample1.txt

```
mem[ 0] = 32'h00000013;
mem[ 1] = 32'h00000033;
mem[ 2] = 32'h000000b3;
mem[ 3] = 32'h00000133;
mem[ 4] = 32'h000001b3;
mem[ 5] = 32'h00000233;
mem[ 6] = 32'h000002b3;
mem[ 7] = 32'h00000333;
mem[ 8] = 32'h000003b3;
mem[ 9] = 32'h00000433;
mem[10] = 32'h000004b3;
mem[11] = 32'h00000533;
mem[12] = 32'h000005b3;
mem[13] = 32'h00000633;
mem[14] = 32'h000006b3;
mem[15] = 32'h00000733;
mem[16] = 32'h000007b3;
mem[17] = 32'h00000833;
mem[18] = 32'h000008b3;
mem[19] = 32'h00000933;
mem[20] = 32'h000009b3;
mem[21] = 32'h00000a33;
mem[22] = 32'h00000ab3;
mem[23] = 32'h00000b33;
mem[24] = 32'h00000bb3;
mem[25] = 32'h00000c33;
mem[26] = 32'h00000cb3;
mem[27] = 32'h00000d33;
mem[28] = 32'h00000db3;
mem[29] = 32'h00000e33;
mem[30] = 32'h00000eb3;
mem[31] = 32'h00000f33;
```

RVCore_Base, RISC-V RV32I Baseline Version v2024-10-22a



```
module m_main (  
    input wire w_clk,      // 100MHz clock signal  
    input wire w_uart_rx,  // UART rx, data line from PC to FPGA  
    output wire w_uart_tx  // UART tx, data line from FPGA to PC  
);
```

```
    wire w_clk50m, locked;  
    clk_wiz_0 clk_wiz1 (w_clk50m, locked, w_clk);  
  
    reg r_rst = 1;  
    always @(posedge w_clk50m) r_rst <= ~locked;  
  
    reg core_rst = 1;  
    always @(posedge w_clk50m) core_rst <= (r_rst | r_done==0);
```

```
    wire w_en;  
    wire [7:0] w_char;  
    m_uart_rx uart_rx1 (w_clk50m, w_uart_rx, w_char, w_en);
```

```
    reg r_done = `DONE_INIT;  
    reg r_we = 0;  
    reg [31:0] r_wcnt = 0, r_adr = 0, r_data = 0;  
    always @(posedge w_clk50m) if (r_done==0) begin  
        if (w_en) begin  
            r_adr <= r_wcnt;  
            r_data <= {w_char, r_data[31:8]};  
            r_we <= (r_wcnt[1:0]==3);  
            r_wcnt <= r_wcnt + 1;  
        end else begin  
            r_we <= 0;  
            if (r_wcnt>=`MEM_SIZE) r_done <= 1;  
        end  
    end  
end
```

```
    wire [3:0] D_WE;  
    wire [31:0] I_IN, I_ADDR, D_IN, D_OUT, D_ADDR;  
    m_rvcore rvcore1 (w_clk50m, core_rst, I_IN, D_IN, I_ADDR, D_ADDR, D_OUT, D_WE);
```

```
    m_imem imem1 (w_clk50m, r_we, r_done ? I_ADDR[11:2] : r_adr[11:2], r_data, I_IN);  
    m_dmem dmem1 (w_clk50m, {4{r_we}} | D_WE, r_done ? D_ADDR[11:2] : r_adr[11:2],  
        r_done ? D_OUT : r_data, D_IN);
```

```
    wire [1:0] tohost_cmd = ((D_ADDR==32'h40008000) && D_WE==4'hf) ? D_OUT[17:16] : 0;  
    wire [7:0] tohost_char = D_OUT[7:0];
```

```
    reg [7:0] ubuf [0:4095];  
    reg [11:0] r_head=0, r_tail=0;  
    always @(posedge w_clk50m) if (core_rst==0 && tohost_cmd==1) begin  
        ubuf[r_tail] <= tohost_char;  
        r_tail <= r_tail + 1;  
    end
```

```
    reg [31:0] r_cnt = 1;  
    always @(posedge w_clk50m) r_cnt <= (r_cnt>(`UART_CNT*12)) ? 1 : r_cnt + 1;
```

```
    wire w_uart_we = ((core_rst==0) && (r_cnt==1) && (r_head!=r_tail));  
    wire w_uart_tx_t;  
    always @(posedge w_clk50m) if (core_rst==0 && w_uart_we) r_head <= r_head + 1;  
    m_uart_tx uart_tx1 (w_clk50m, w_uart_we, ubuf[r_head], w_uart_tx_t);
```

```
    always @(posedge w_clk50m) begin ///// for simulation  
        if (tohost_cmd==1) $write("%c", tohost_char);  
        if (tohost_cmd==2) begin  
            $write("simulation finished.\n");  
            $finish();  
        end  
    end  
endmodule
```

proc.v

RVCore_Base, RISC-V RV32I Baseline Version v2024-10-22a

```
module m_uart_tx (
    input wire      w_clk,    // 50MHz clock signal
    input wire      w_we,    // write enable
    input wire [7:0] w_din,   // data in
    output wire      w_uart_tx // UART tx, data line from FPGA to PC
);
    reg [8:0] r_buf = 9'b1_1111_1111;
    reg [7:0] r_cnt = 1;
    always @(posedge w_clk) begin
        r_cnt <= (w_we) ? 1 : (r_cnt==`UART_CNT) ? 1 : r_cnt + 1;
        r_buf <= (w_we) ? {w_din, 1'b0} : (r_cnt==`UART_CNT) ? {1'b1, r_buf[8:1]} : r_buf;
    end
    assign w_uart_tx = r_buf[0];
endmodule
```

```
module m_uart_rx (
    input wire      w_clk,    // 100MHz clock signal
    input wire      w_rxd,    // UART rx, data line from PC to FPGA
    output wire [7:0] w_char,  // 8-bit data received
    output reg      r_en = 0 // data enable
);
    reg [2:0] r_detect_cnt = 0; /* to detect the start bit */
    always @(posedge w_clk) r_detect_cnt <= (w_rxd) ? 0 : r_detect_cnt + 1;
    wire w_detected = (r_detect_cnt>2);

    reg      r_busy = 0; // r_busy is set while receiving 9-bits data
    reg [3:0] r_bit  = 0; // the number of received bits
    reg [7:0] r_cnt  = 0; // wait count for 1Mbaud
    always@(posedge w_clk) r_cnt <= (r_busy==0) ? 1 : (r_cnt==`UART_CNT) ? 1 : r_cnt + 1;

    reg [8:0] r_data = 0;
    always@(posedge w_clk) begin
        if (r_busy==0) begin
            {r_data, r_bit, r_en} <= 0;
            if (w_detected) r_busy <= 1;
        end
        else if (r_cnt>= `UART_CNT) begin
            r_bit <= r_bit + 1;
            r_data <= {w_rxd, r_data[8:1]};
            if (r_bit==8) begin r_en <= 1; r_busy <= 0; end
        end
    end
    assign w_char = r_data[7:0];
endmodule
```

proc.v